

60 GHz DEMONSTRATOR

TEAM LEAD: LEONARDO GOMES – PHD CANDIDATE


JOÃO LÉ – MSC CANDIDATE

LUIS CARTAGENA – PHD CANDIDATE

WALTER ARANDA – MSC CANDIDATE


MOTIVATION

- We don't intend to design cutting-edge, state-of-the-art mmWV circuits here, but instead we want to fulfill two goals:
 - Prove that it is possible to design mmWV circuits in an open-source environment
 - Help the community by developing a (rough) OS RFIC design flow
- To this end, we propose submitting some of the necessary building blocks of any transceiver, turning the Caravel user area into a mini MPW:
 - Amplifiers: PA, LNA, VGA
 - Oscillator: VCO
 - RF switch
 - Balun and slow-wave line for impedance matching and low-loss interconnections
 - Standalone, diceable test circuits for RF MOSFET and Cascode

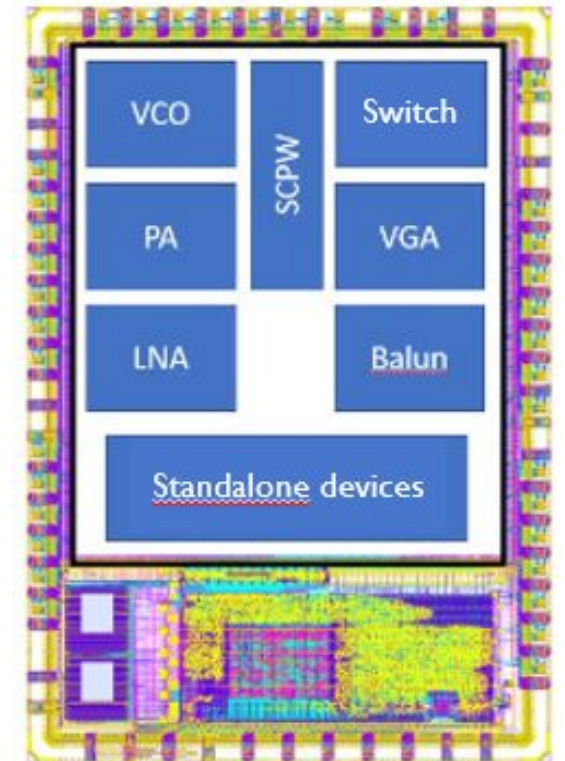


MOTIVATION

 - A VCO is one of the most important building blocks for a RF transmission system, and is a good testbench for the quality of passive devices and of the active devices (MOSFETs)
- A VGA is very useful in a RF front-end to avoid saturation of the stages behind the LNA and to suppress sidelobes in beam-steering antenna arrays




Voltage-Controlled Oscillator - VCO

 - Cross-coupled pair-based VCO, lumped LC tank
 - Single-turn planar inductor, differential varactor bank to control the oscillation frequency
- CCP biased by a basic current mirror
 - Class A operation
- Push-push topology
 - 2nd harmonic is taken from the inductor center tap
 - Output will be matched to the 50-ohm RF pad
 - Tank resonates at 30 GHz




VCO

- CCPVCO is a proven oscillator design that sees widespread use in monolithic applications
- However, the performance is limited by the Q-factor of the varactor bank
- Design at a lower current density (0.15 mA/ μm)
 - Produces larger fets with larger parasitic capacitance, but is safer as the biasing can be extended to augment loss compensation if the oscillations don't start
- Design uses RF MOSFET cells (aF08VW0p84L0p15)
 - Modular nature of the devices makes the design flow easier since the high-frequency effects are already included in the spice model

 


VCO

- Current mirror is a simple design, using two matched MOSFETs
 - Has lower output impedance than a cascode mirror
 - But offers more headroom
 - The available headroom for the current mirror is small, because most of the V_{dd} voltage has to fall on the CCP to maximize RF power output
- $L = 150\text{nm}$
 - Try to get a high AC output impedance
 - Larger $L \rightarrow$ smaller f_t and larger required V_{ov}

 


VCO

- Varactor bank, differential configuration
 - Varactor gate tied to the 1.8V supply
 - Biasing done through the source/drain contacts via a high-resistivity poly resistor
- Low Q-factor is the main design constraint for the VCO
 - And the main driving factor for the push-push topology
- Goal: find a W,L set that offers a minimum Q above 4 and a capacitance tune about 1
 - $C_{tr} = (C_{max} - C_{min}) / C_{nominal}$
 - And use multiple cells in parallel to arrive at a better-performing bank than a single, large varactor

 


VCO

 - Inductor
- Designed in ASITIC, verified in commercial tools
 - Equivalent PI model used in ngspice simulation




VCO

 - Output matching
- SCPW designed using commercial tools
 - High Q-factor minimizes power loss
 - Equivalent RLRC model used in ngspice simulation




VCO - RESULTS


- CCP: 4 RF fets in parallel biased at $0.15 \text{ mA}/\mu\text{m}$
 - Total W of $26.88 \mu\text{m}$, current consumption of 8 mA for the two fets
 - Maximum bias current of $0.35 \text{ mA}/\mu\text{m}$ (18.9 mA)
- Current mirror: $W = 100 \mu\text{m}$, $L = 150 \text{ nm}$
- Varactor bank: 35 units of $W = 1.5 \mu\text{m}$, $L = 180 \text{ nm}$
 - Two banks required for differential operation
- Inductor: $W = 10 \mu\text{m}$, $D = 130 \mu\text{m}$
 - Custom $\text{LI}+\text{P}+$ guard ring included in the design, no ground shield

 


VCO - RESULTS

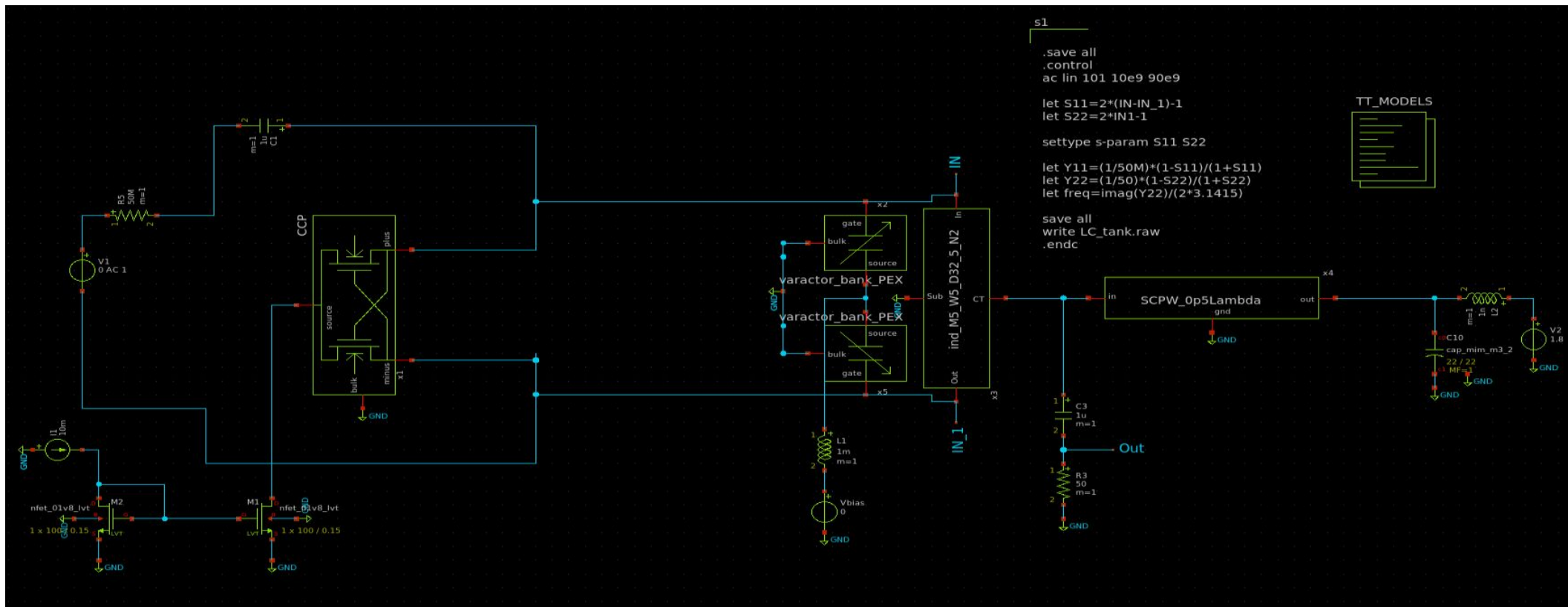



VCO - RESULTS

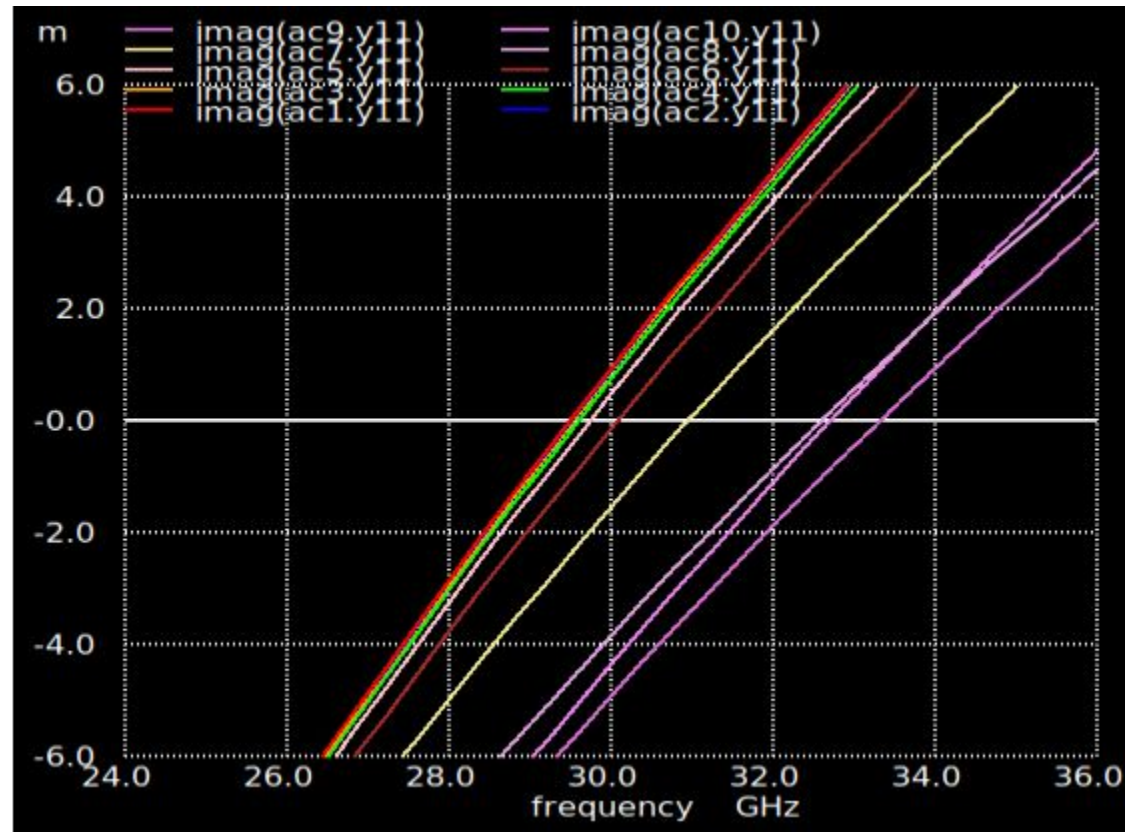



VCO - RESULTS

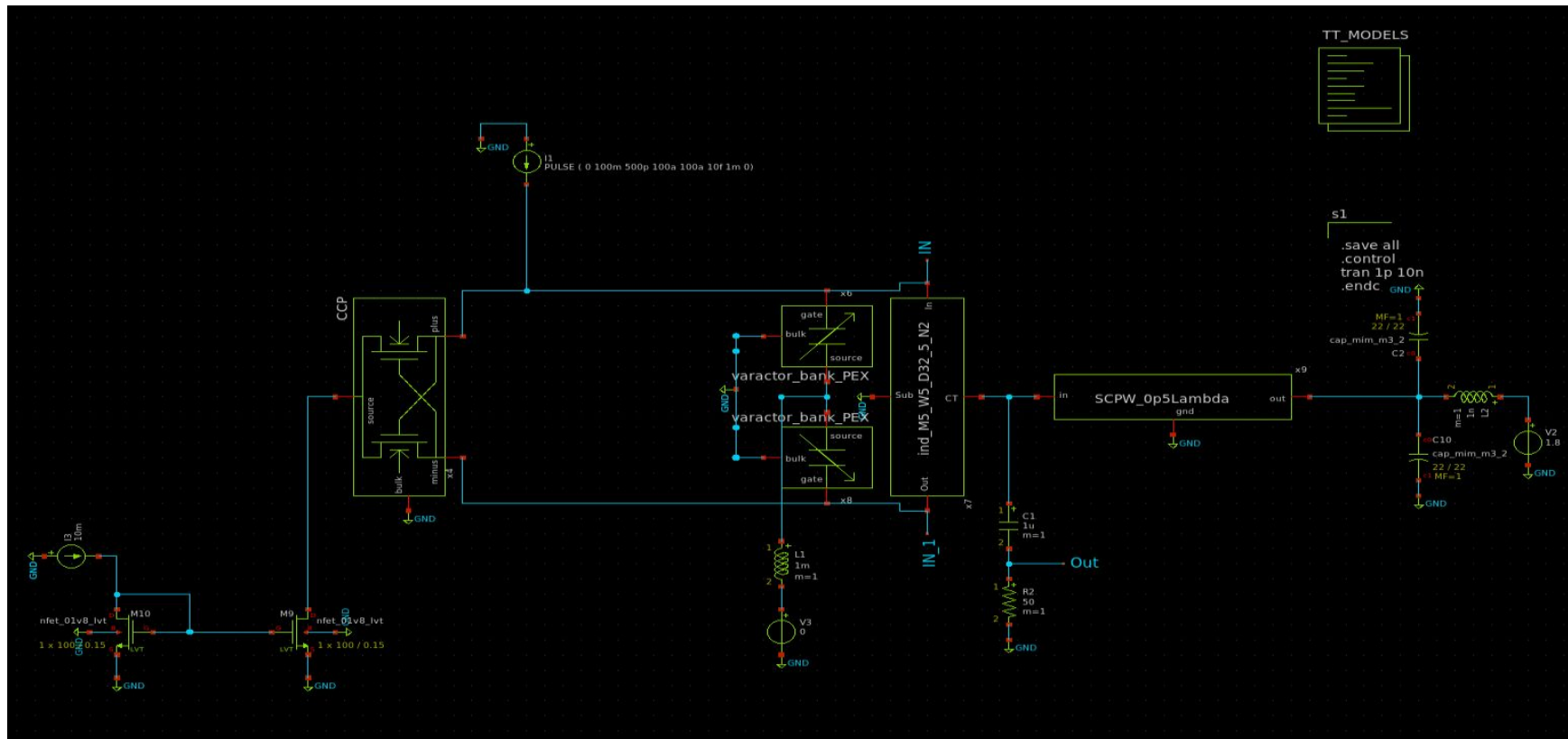


VCO - RESULTS

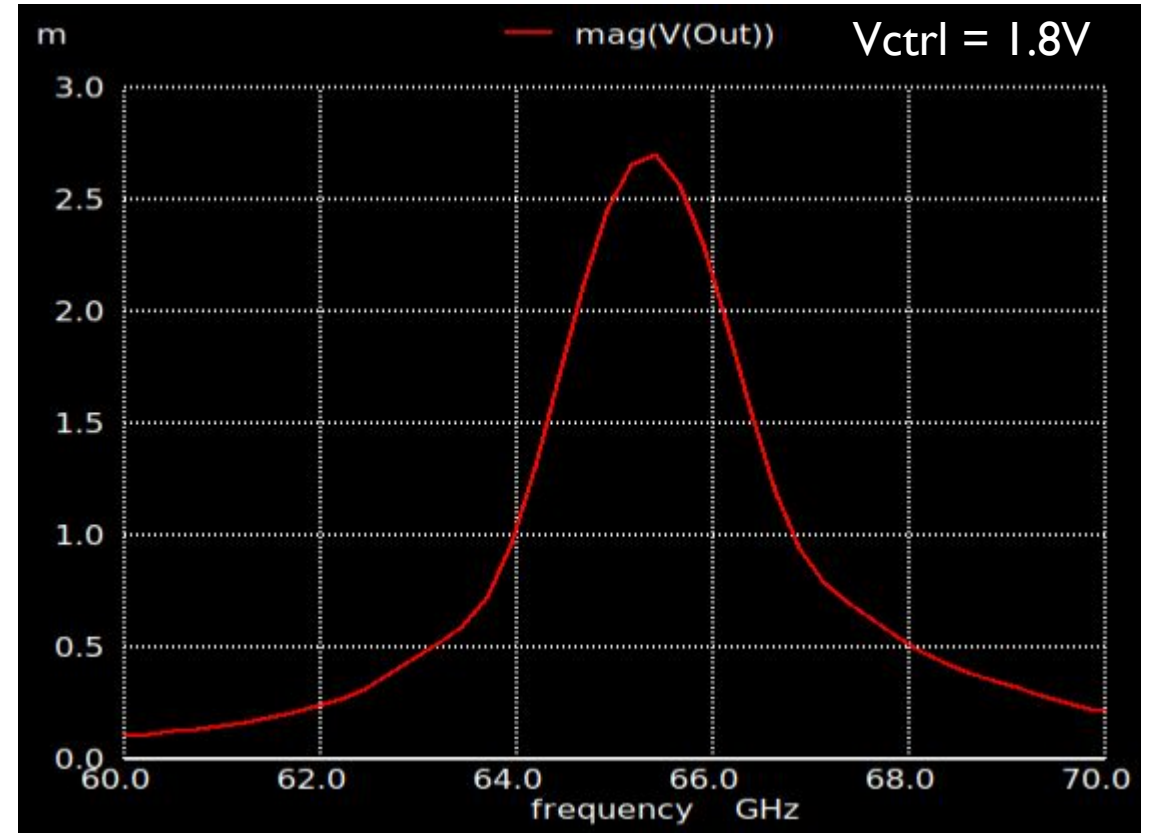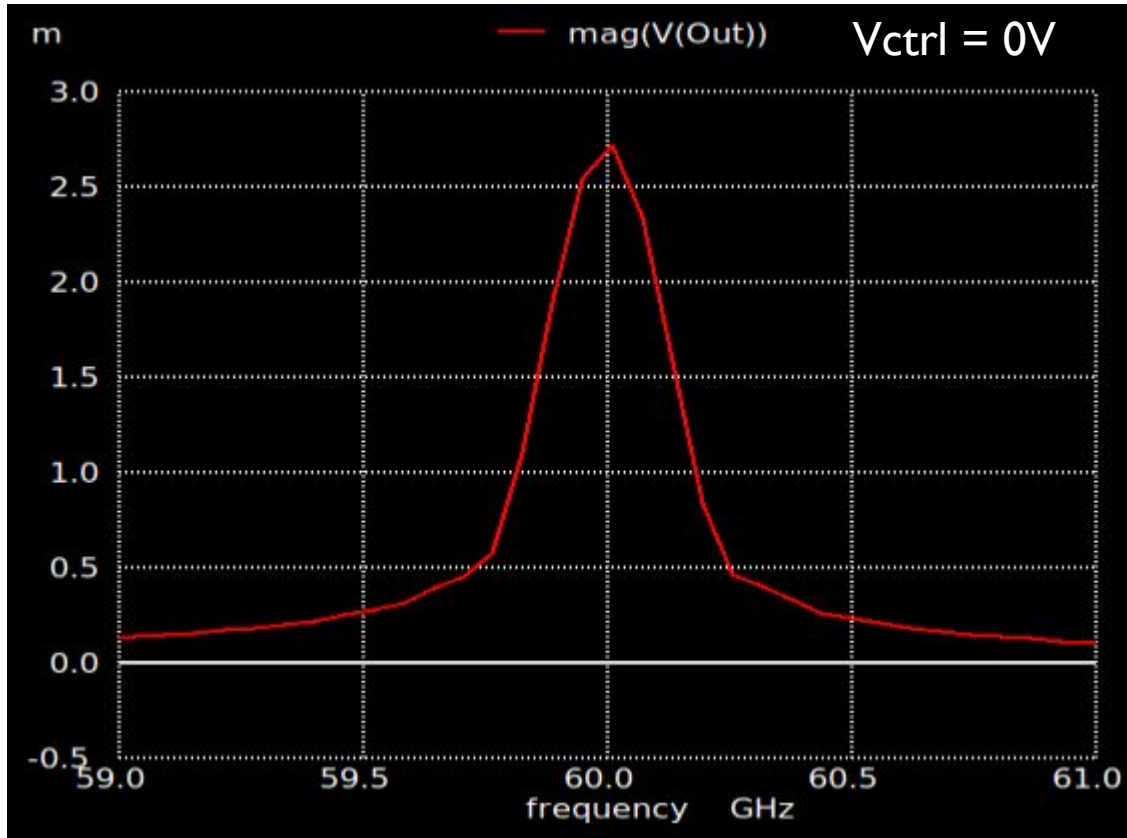


VCO - RESULTS

 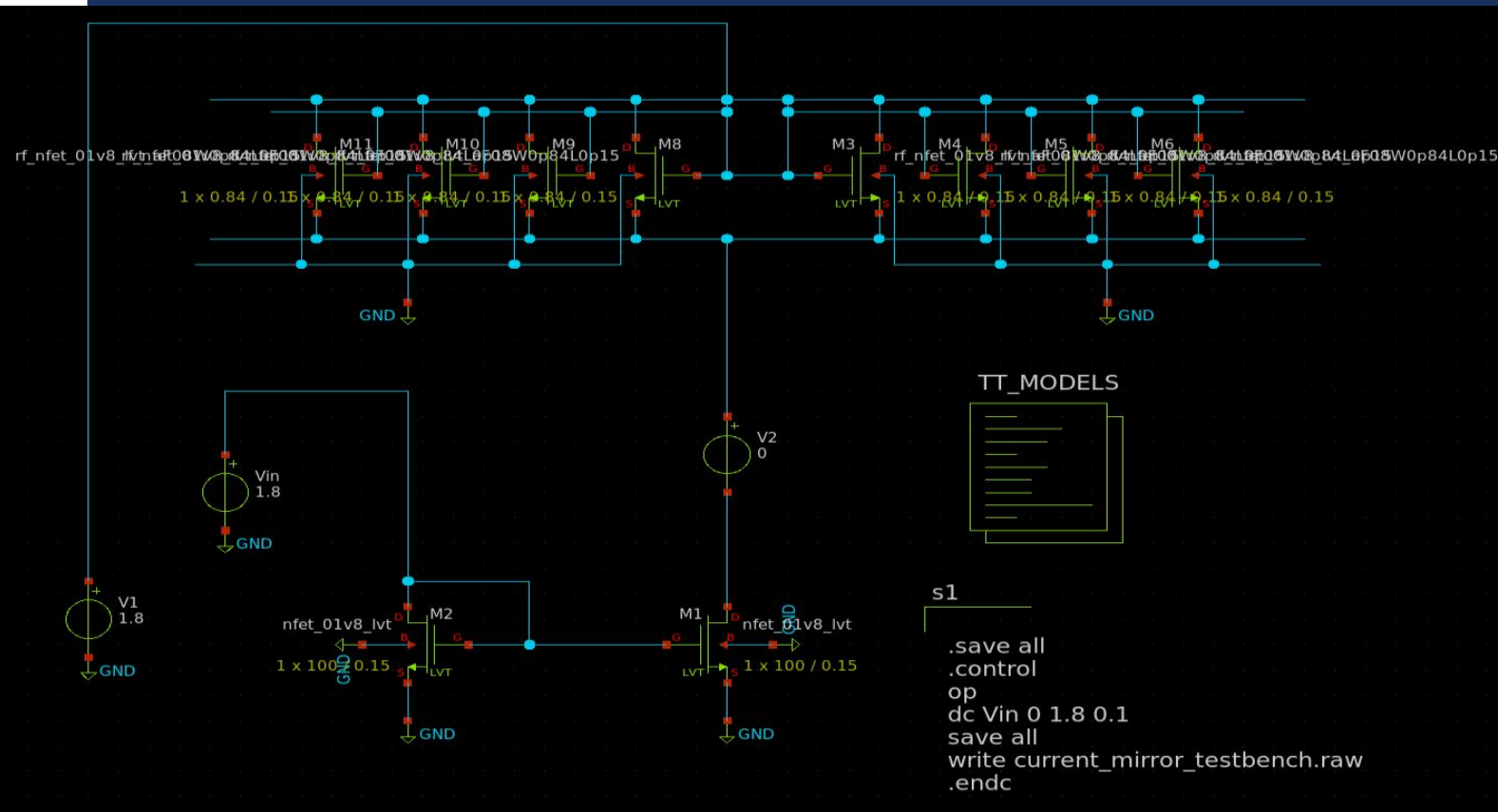


VCO - RESULTS

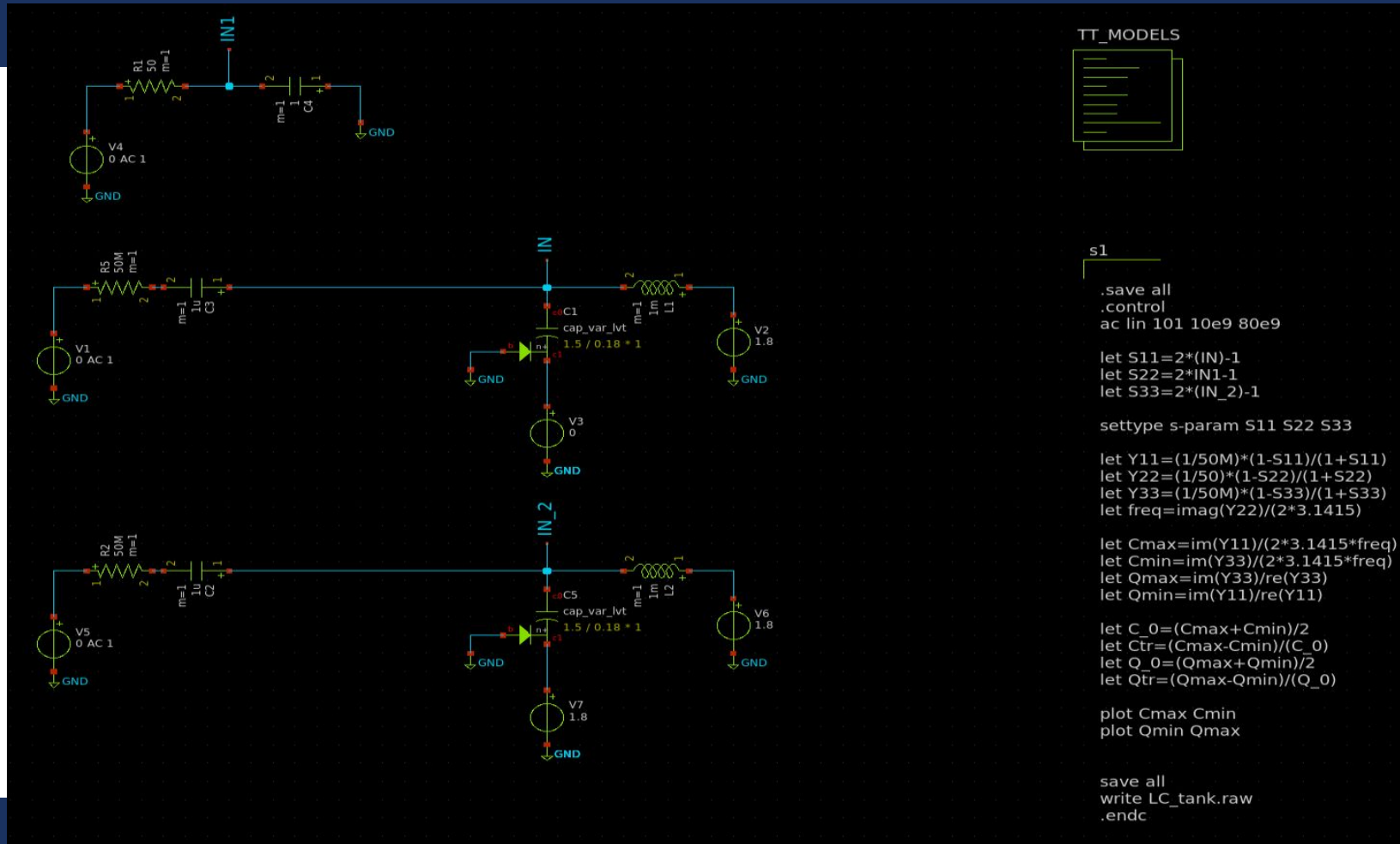


VCO - RESULTS

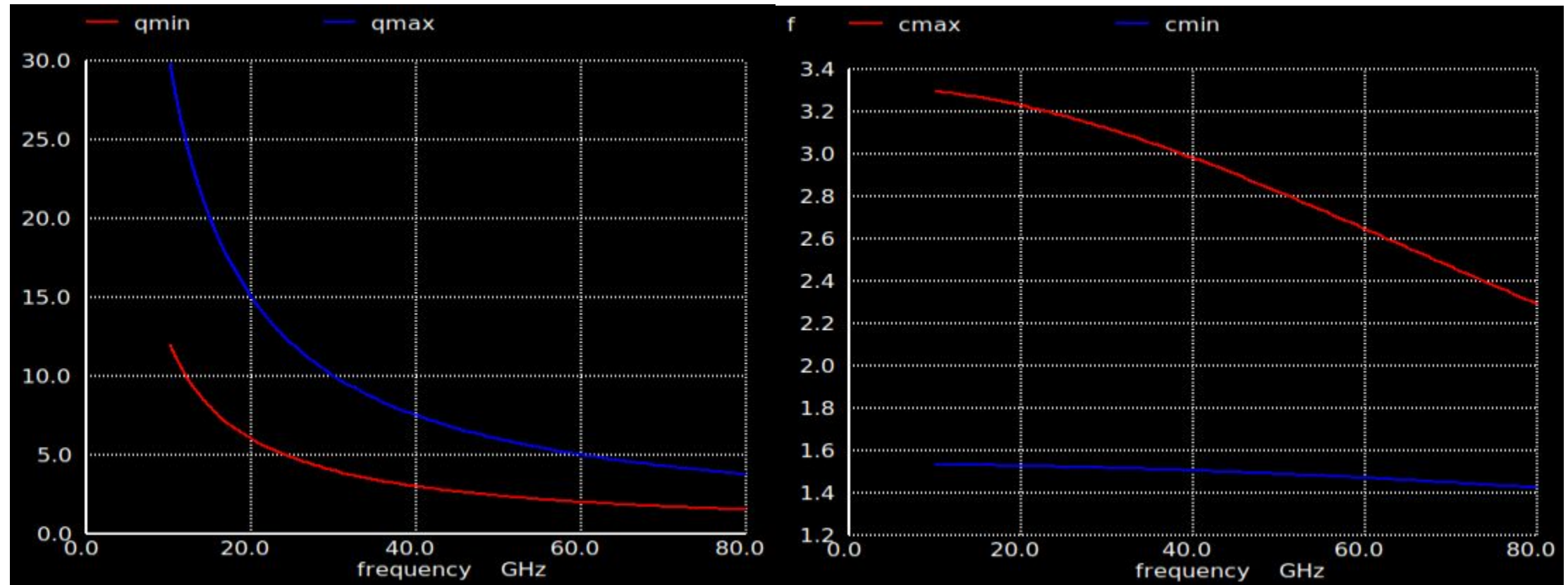

VCO - RESULTS

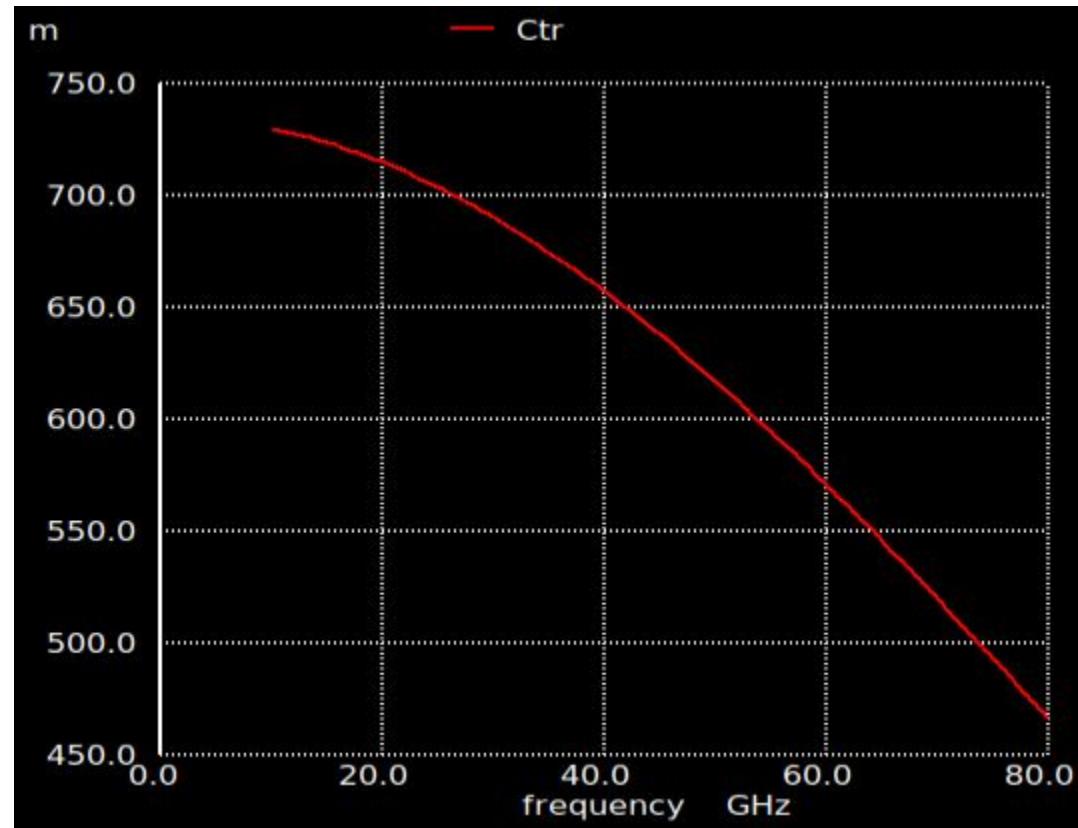


VCO - RESULTS

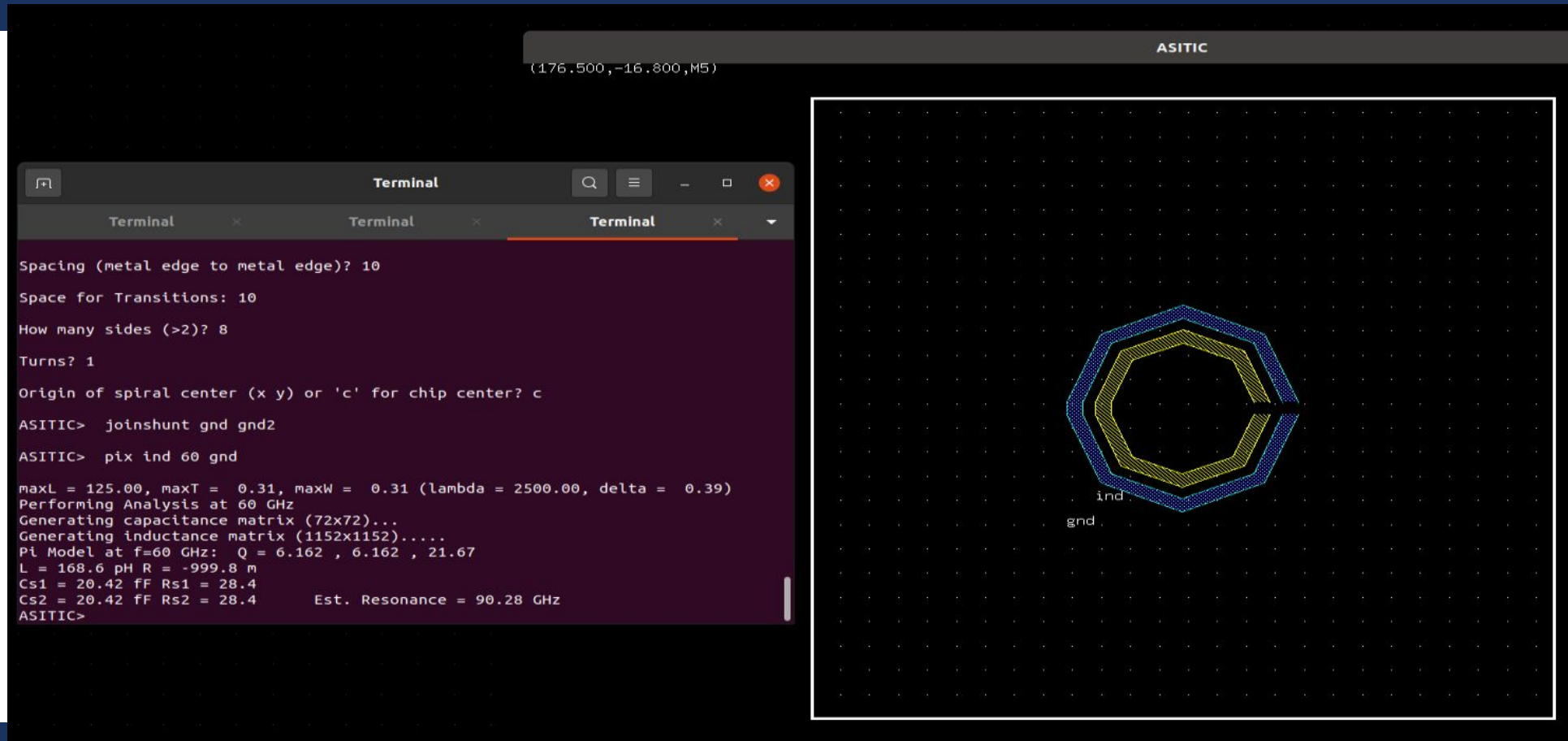


VCO – UNSIMULATED PARTS

 - Output matching need to be done
- Plan: create a new testbench to measure the output reflection coefficient (S_{11} in a 1-port setup) and design a conjugate matching network




VCO – RESULTS VERSUS INITIAL GOALS

 - Initial specs
 - 3 GHz tuning range at 60 GHz
 - Phase noise better than -100 dBc/Hz at 10 MHz offset from the carrier frequency
 - 18 mW of DC power consumption (VCO core only)
 - Maximum DC power consumption of 36 mW
 - Buffer with input capacitance smaller than 6 fF, output reflection loss smaller than 10 dB inside the V-band.




VCO – RESULTS VERSUS INITIAL GOALS

 - Schematic level simulation specs
 - 5.7 GHz tuning range at 60 GHz
 - No phase-noise simulation capability
 - 14.4 mW of DC power consumption (VCO core only)
 - Maximum DC power consumption of 34 mW
 - No buffers needed




Variable Gain Amplifier - VGA

- Current-steering cascode topology
 - When $V_{ctrl} = 0$, M3 is off and the gain is maximum
 - When $V_{ctrl} = 1.8V$, M3 is on and shunts M2, gain is minimum
 - Since the drain current of M2 isn't disturbed, and because of the good IO isolation of the cascode topology, the output impedance isn't affected
- V_{gg} bias M1 and sets the maximum gain of the circuit
 - $V_{gg} = 1V$ results in maximum f_t
- Input and output impedance matching networks

 


VGA

 - Current-steering cascode is a simple, yet capable topology
 - Easier to implement than a Gilbert cell, as it doesn't need baluns and has fewer transistors
 - But is more prone to noise and to phase variation with V_{ctrl}
- A simpler design maximizes the chances of success, as there are too many unknowns for the RF designers




VGA

- Design procedure: find the ratio of W_{M1} and W_{M2} that maximizes the Maximum Available Gain (MSG)
 - Fixing $W_{M3} = W_{M2}$
- Design the output and input matching networks
 - MIM capacitors, TLine stubs to realize series drain load
 - S-CPW transmission line to minimize losses, and thus improve the amplifier gain
 - Single-frequency matching at 60 GHz
- RF_in and RF_out are the input and output of this amplifier, to be supplied by custom Ground-Signal-Ground pads

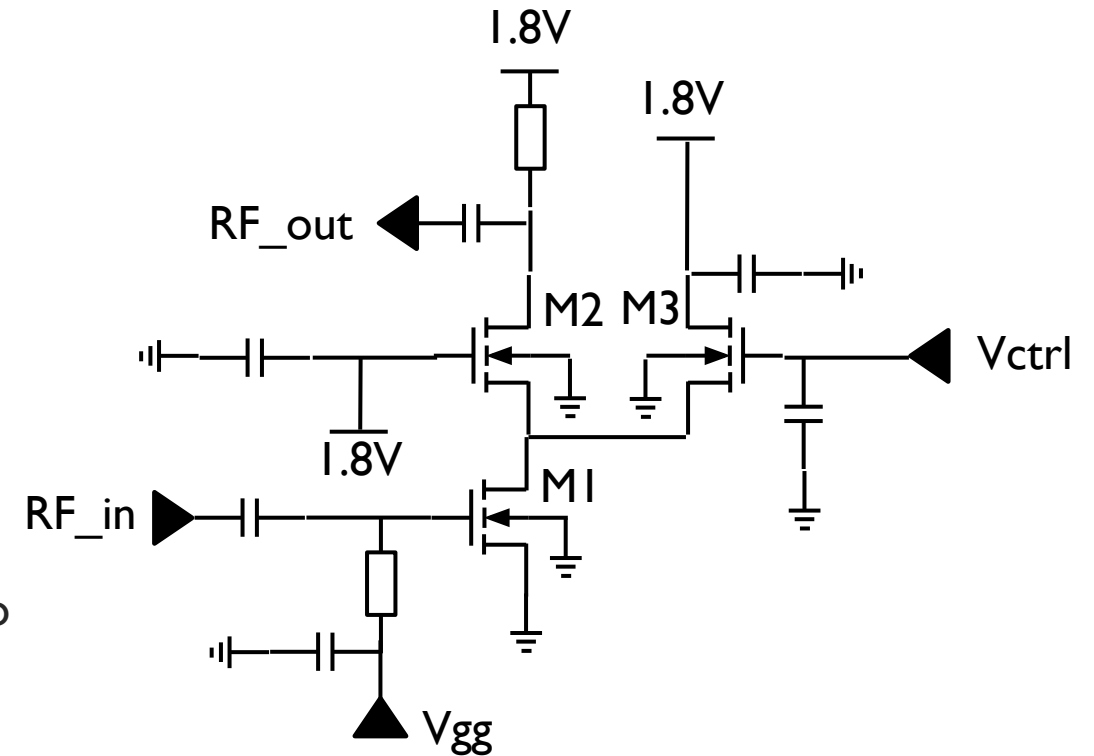


VGA

 - MOSFET model: standard Pcell model with added series resistor to the gate to model non-quasi-static effects
- Instead of using the RF MOSFET cells...
 - Fixed cells make running parametric sweeps more difficult
 - The nqs resistor improves the accuracy in mmW frequencies




VGA

- Design steps for the amplifier core:
 - Xschem: built a testbench to run S-parameter simulations and export a s2p file
 - Design the input and output matching networks in commercial tools
 - Verification in xschem, generate the schematic netlist
 - Klayout: layout of the cascode transistor plus DC decoupling capacitors and DRC check (to be verified in Magic)
 - Netgen: LVS
 - Magic: parasitic extraction
 - Xschem: PLS

 


VGA - RESULTS

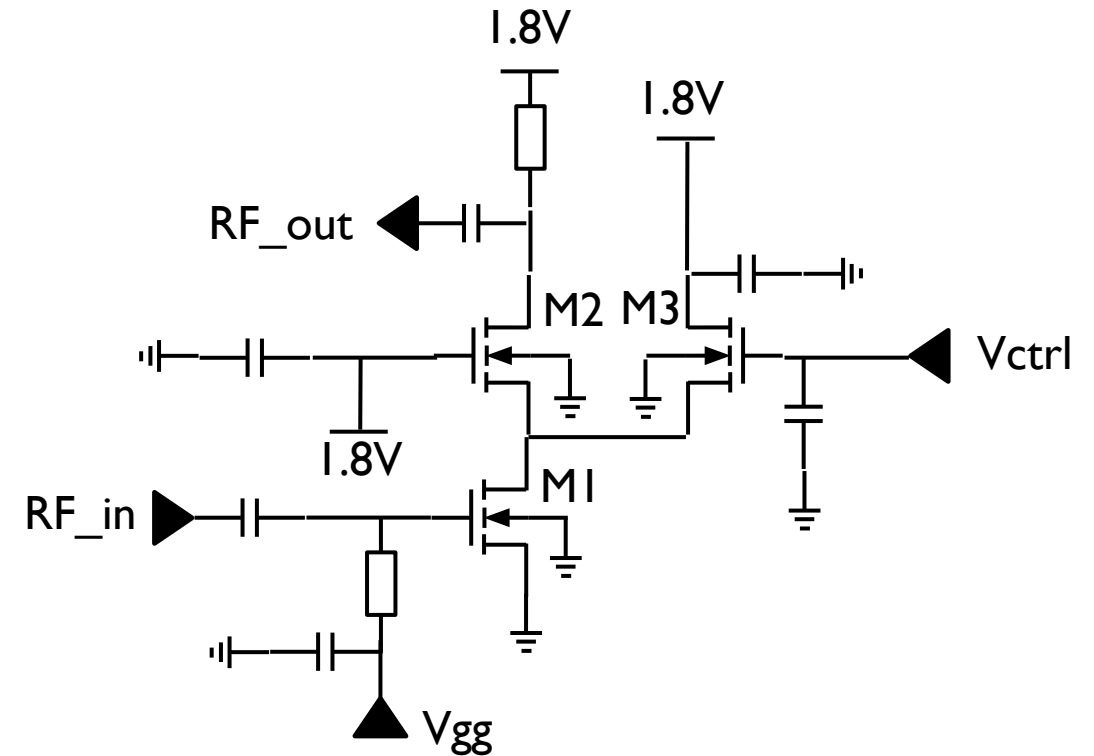- Drain stub length = 280.45 μm , out capacitor 2.85 μm x 2.85 μm
- Gate stub length = 198.8 μm , in capacitor 4.4 μm x 4.4 μm
- $W_{M1} = W_{M2} = W_{M3} = 25.2$ μm , L is fixed at 130 nm
- MOSFETs laid out as multifinger devices, $W_{\text{finger}} = 840$ nm
 - N_f , thus, equals 30 for all devices
- DC current of 2.95 mA at maximum gain
 - 3 mA at minimum gain




VGA - RESULTS



S-matrix export with nqs modelling

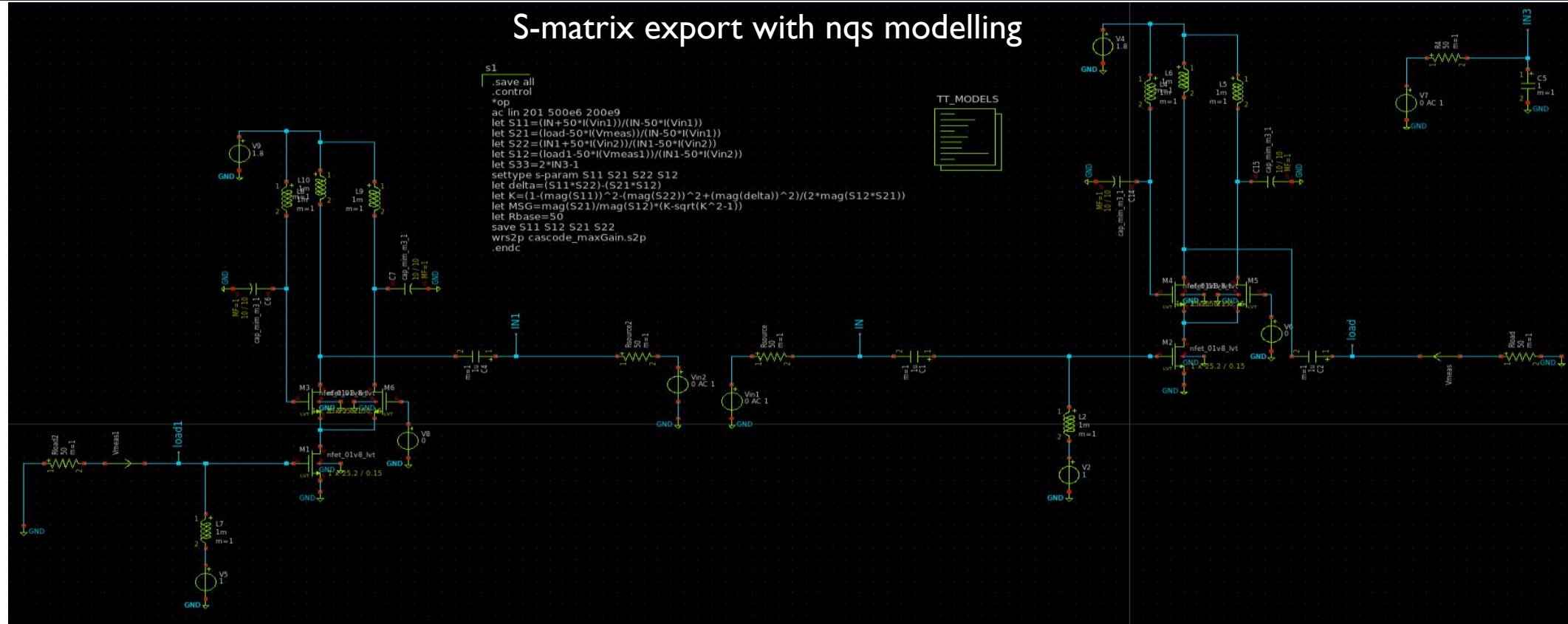

VGA - RESULTS

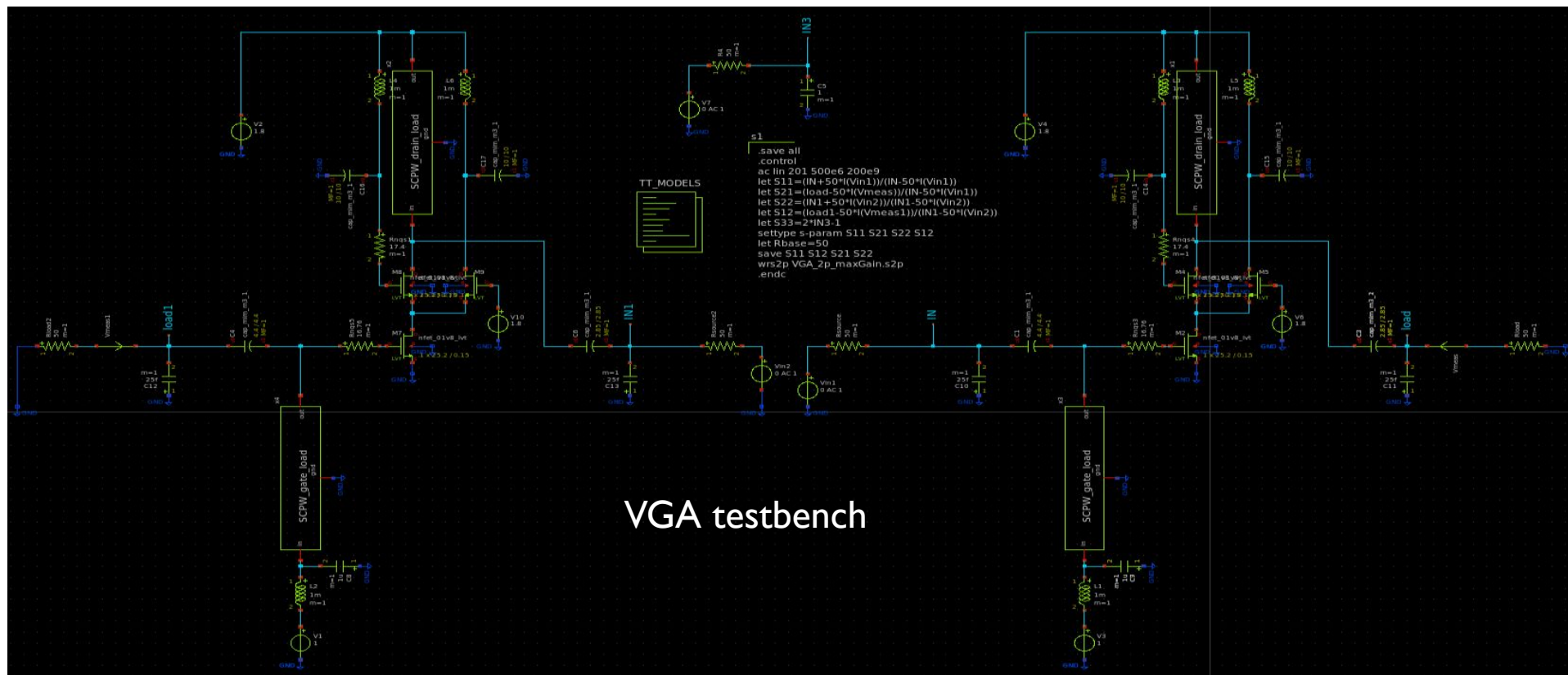


VGA - RESULTS

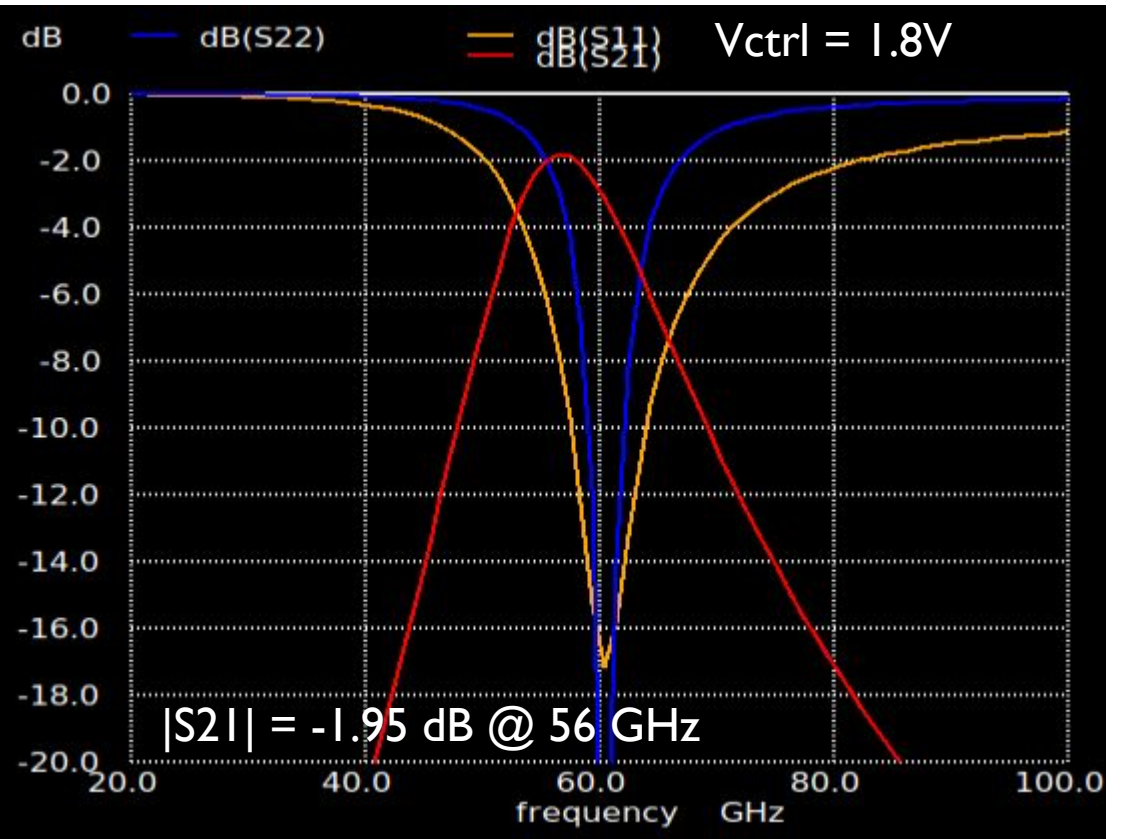 


VGA - RESULTS

 - 1.8V and ground will be supplied externally via one of the Caravel analog IO pins
- V_{gg} and V_{ctrl} will be supplied via Caravel GPIO used as analog pin
- Circuit will share 1.8V and V_{gg} pins with the LNA and PA, reducing the pin count to better accommodate all designs inside the user area
- RF pads plus accesses will be laid out inside the user area




VGA – UNSIMULATED PORTIONS

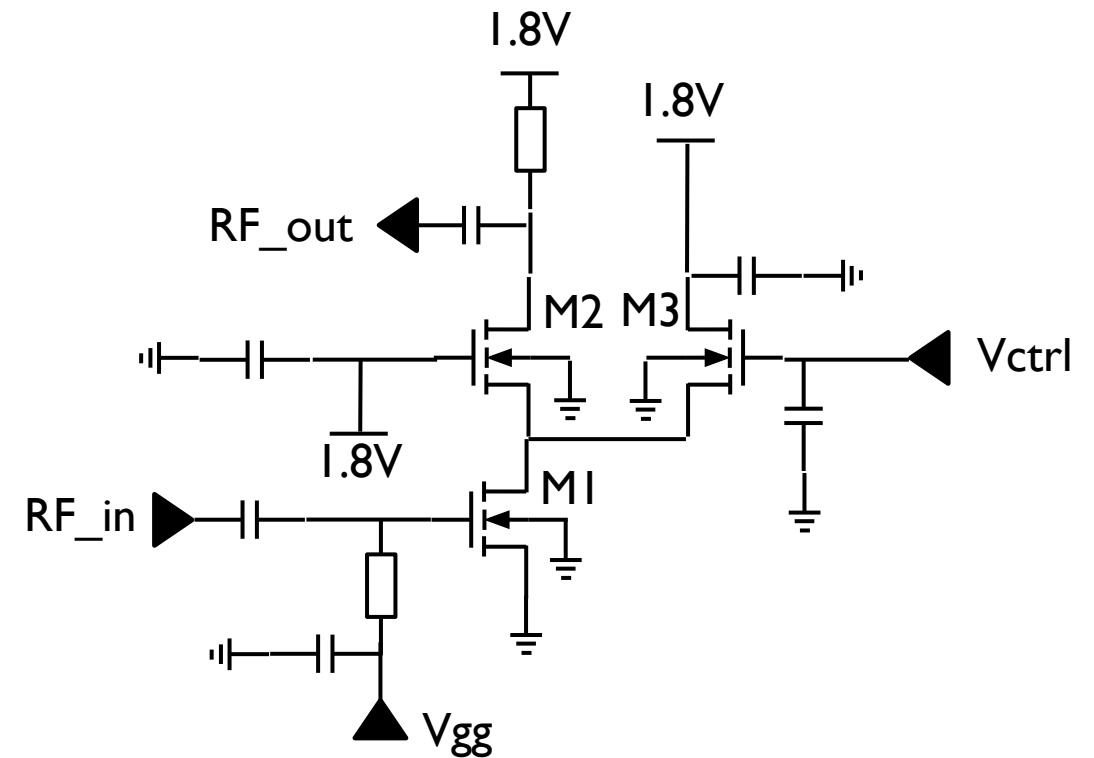- To-do: harmonic balance simulation to extract the non-linear behavior of this circuit
- AKA the 1 dB compression point and the 3th harmonic intercept points
- Plan: use ngspice script to run a nested .tran simulation, apply fft, measure the mag() of the fundamental and plot it against the input RF power




VGA – RESULTS VERSUS INITIAL GOALS

 - Initial specs:
 - Maximum gain of 10 dB
 - Gain control range better than 20 dB (from -10 dB to +10 dB)
 - 10dB input and output bandwidth of 15% centered at 60 GHz
 - Typical DC power consumption of 20 mW per cell, maximum of 40 mW
 - Output 1dB compression point of -20 dBm.



VGA – RESULTS VERSUS INITIAL GOALS

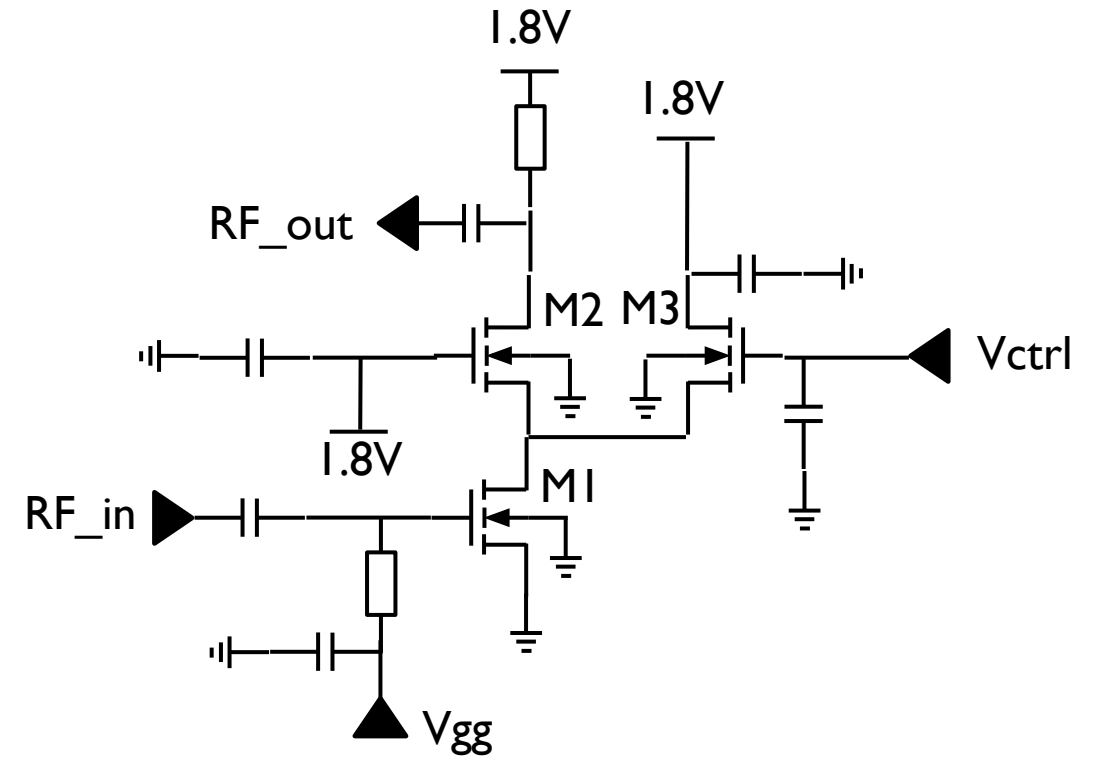- Schematic level simulation specs:
 - Maximum gain of 1.94 dB
 - Gain control range of 3.89 dB
 - 10dB input and output bandwidth of 5% centered at 60 GHz
 - Typical DC power consumption of 5.4 mW



Balanced to Unbalanced Transformer - BALUN


On-chip transformers are versatile components. They are commonly used as two- or three-port devices for impedance conversion, circuit isolation (DC decoupling, common mode rejection or RF chokes) or/and BALanced-to-UNbalanced (and vice versa) signal conversion. These characteristics make this element very common in building or connecting basic active blocks with the rest of the circuit of a millimeter-wave front-end.

In simulations, we can measure it as a two port device: one of them differential and the other single ended. That way, we can express the performance looking to the transmission (insertion loss) and reflected power (return loss).


BALUN

- Using a well-known octagonal winding shape, we created a coplanar waveguide structure;
- The primary is single-ended and is placed on metal 5; the secondary is differential and is in metal 4;
- The trace width is 4 μm and the radius of the loop is approx. 80 μm ;

 Next step is to insert the RF pads into this layout.



BALUN - results

 

Slow-wave Transmission Line

A Coplanar Waveguide (CPW) transmission line was developed; by periodically adding transverse metal strips, placed over metal 2, it is possible to create a slow wave effect, in addition to preventing the electric field from penetrating the silicon.

Our goal is to get a 50 Ohm transmission line with the highest quality factor (Q).

Dimensions:


Trace signal width: 24.4 μ m

Trace ground width: 41.55 μ m



Distance between above traces: 27.4 μ m

Width of metallic strips: 0.45 μ m

Metallic strips spacing: 3.1 μ m

 

Slow-wave Transmission Line - results

  


Slow-wave Transmission Line - results

The Quality Factor (Q) of a transmission line is a measure of how much energy the device stores in relation to how much it dissipates.

The figure on the side shows the Q of this line, which is calculated from the S parameters.

```
A      (((1+S11corr)*(1-S11corr)+S12cor*S12cor))/(2*S12cor)
B      50*(((1+S11corr)*(1+S11corr)-S12cor*S12cor))/(2*S12cor)
C      1/50*(((1-S11corr)*(1-S11corr)-S12cor*S12cor))/(2*S12cor)
Q      beta/(abs(2*re(gamma)))
S11corr (S11+S22)/2
S12cor (S12+S21)/2
Zc      sqrt(B/C)
beta     abs(teta/(silicon_J-dem*2))
er_eff   (3e8*beta/(2*pi*freq))^2
gamma    Acosh(A)/(silicon_J-2*dem)
teta     if(cang_rad(S12cor)>0,cang_rad(S12cor)-3.1415,cang_rad(S12cor))
```

 

Instead of the detector.. a switch


Our goal with the detector was to sample the forward signal. However, we didn't notice that sampling the signal without a directional coupler would measure the standing wave voltage (VSWR) at line point, and this changes as the load (or RF probe) changes. In general, directional couplers are implemented as distributed devices (transmission lines) using microwave techniques, which take up a considerable amount of space on the chip (proportional to the guided wavelength).

Therefore, we prefer not to implement this device. In this place, we will implement a Double Pole Single Throw (DPST) switch, which is very useful in adaptive circuits. Our device will be designed to be use in the front-end of a communication electronics device, allowing the same antenna to be shared between transmit and receive.

Switch - schematic

Notice that:

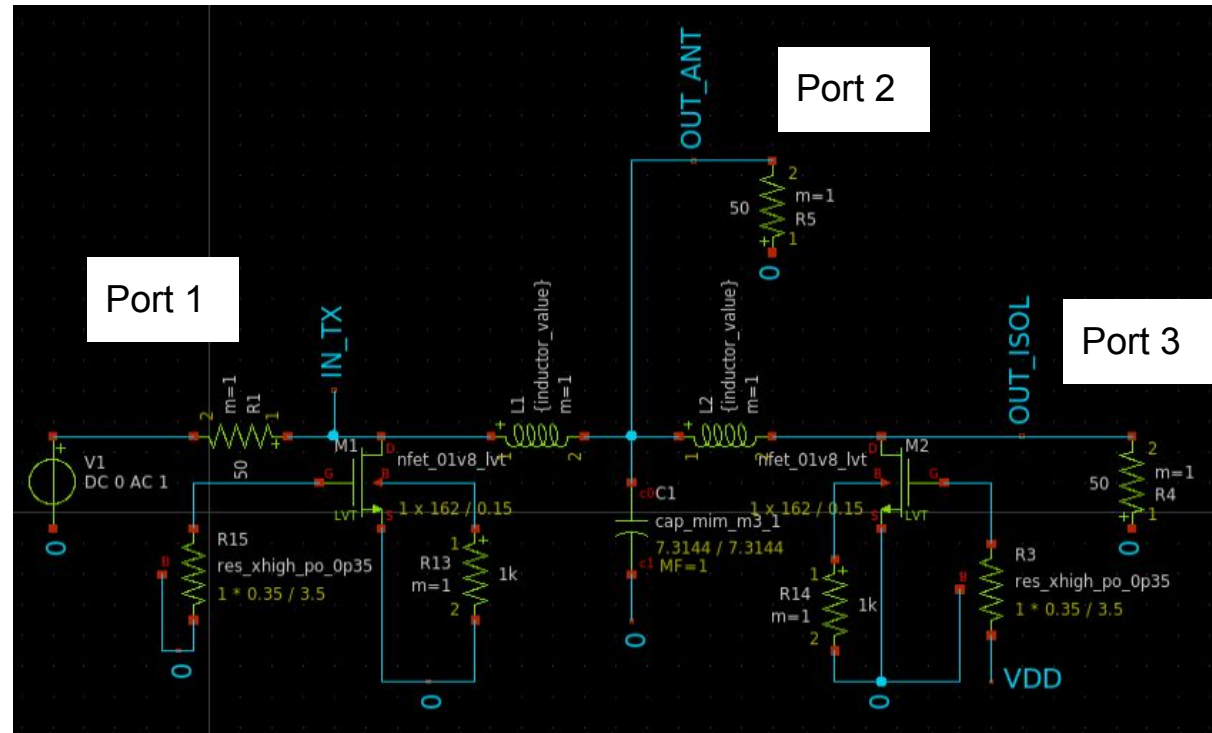- signal leaving the circuit (IN_TX node) is divided between two paths: antenna (OUT_ANT) and isolation (OUT_ISOL) path.
- the directivity is measured as the $S(2,1)$ parameter and must be maximized. The isolation, $S(3,1)$, and should be minimized.




Switch - design flow

- The circuit was based on reference [A7];
- First, the off-capacitance and on-resistance per unit width of the transistor was estimated using the low-voltage 1.8V NMOS PDK MOSFET model; the formulas of the article give us a start point for the value of capacitance and inductances;
- Several Parameter Sweep Simulations were performed to obtain the final results for the components; this step would have been easy if we had been able to use ASCO optimization software;
- All simulations were analyzed of small AC signals, which were then transformed into parameter values. The next objective is to perform a power sweep to see the 1 dB compression point of this switch.

Switch - results

For the reception path, the simulation shows:

 - return loss > 10dB for the range of 45 to 75 GHz;
- maximum insertion loss of 1.45 dB@~60GHz;
- minimum insertion loss for the 60 GHz ISM of 1.7 dB.



Switch - results

For the transmission path, the simulation shows:

- return loss > 10dB for the range of 38 to 99 GHz;
- maximum insertion loss of 1.43 dB@~60GHz;
- minimum insertion loss for the 60 GHz ISM of 2.1 dB.




Switch - results

This figure shows the $S(I,I)$ simulation from 50 MHz to 100 GHz and is put here to show the ngspice plotting capacity.

```
.param inductor_value=105p
*.param capacitor_value=107f
.save all
.control
op
ac lin 801 50e6 100e9
let txS11=2*IN_TX-1
let txS21=2*OUT_ANT
let txS31=2*OUT_ISOL

let rxS11=2*IN_ANT-1
let rxS21=2*OUT_RX
let rxS31=2*OUT_I_ISOL

plot rxS11 txS11 smithgrid
.endc
```

 

Switch - state of the art

References	[S1]	[S2]	[S3]	[S4]	[S5]	[S6]	This work, for a while
Technology	90nm CMOS	65nm CMOS	90nm CMOS	65nm CMOS	55nm CMOS	55nm CMOS	130nm CMOS
Frequency [GHz]*	50-94	58-85	60-110	94-110	85-95	70-100	45-75
Max. Insertion [dB]	3.3	1.8	3-4	4.2	3.2 (TX) 3.6 (RX)	3.5	1.43
Max. Isolation [dB]	27	22	25	25	25 (TX) 20 (RX)	18	~25

* Measure as >10 dB return loss

Power Amplifier - PA

The PA consist of three single-ended, common-source stages biased in class A.


The first stage is biased at the peak f_{max} bias of $0.2\text{mA}/\mu\text{m}$ to maximize gain while its source degeneration inductance is set to $L_S = Z_0/2\pi fT$ for $50\text{-}\Omega$ matching. The second and third stages are biased at the optimum linearity current density of $0.28\text{ mA}/\mu\text{m}$. The transistor width and bias current of the last stage are derived from load-line theory.

PA

Application: high data-rate wireless transmission
and mm-wave sensors


Main characteristics requirements:

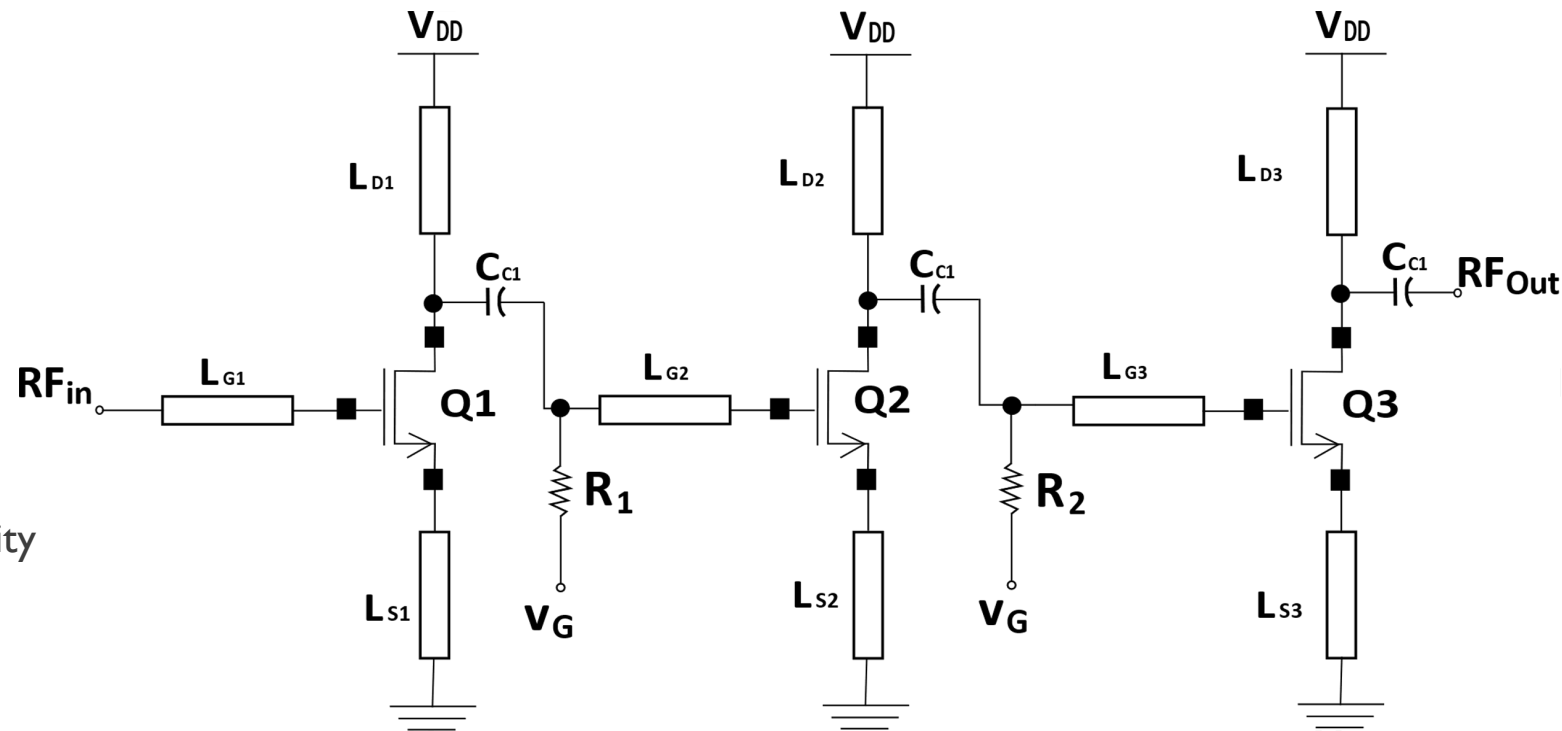- Class A, 3-stage CS topology
- Input /Output match 50Ω
- Branch currents scaled for optimal linearity



PA - results

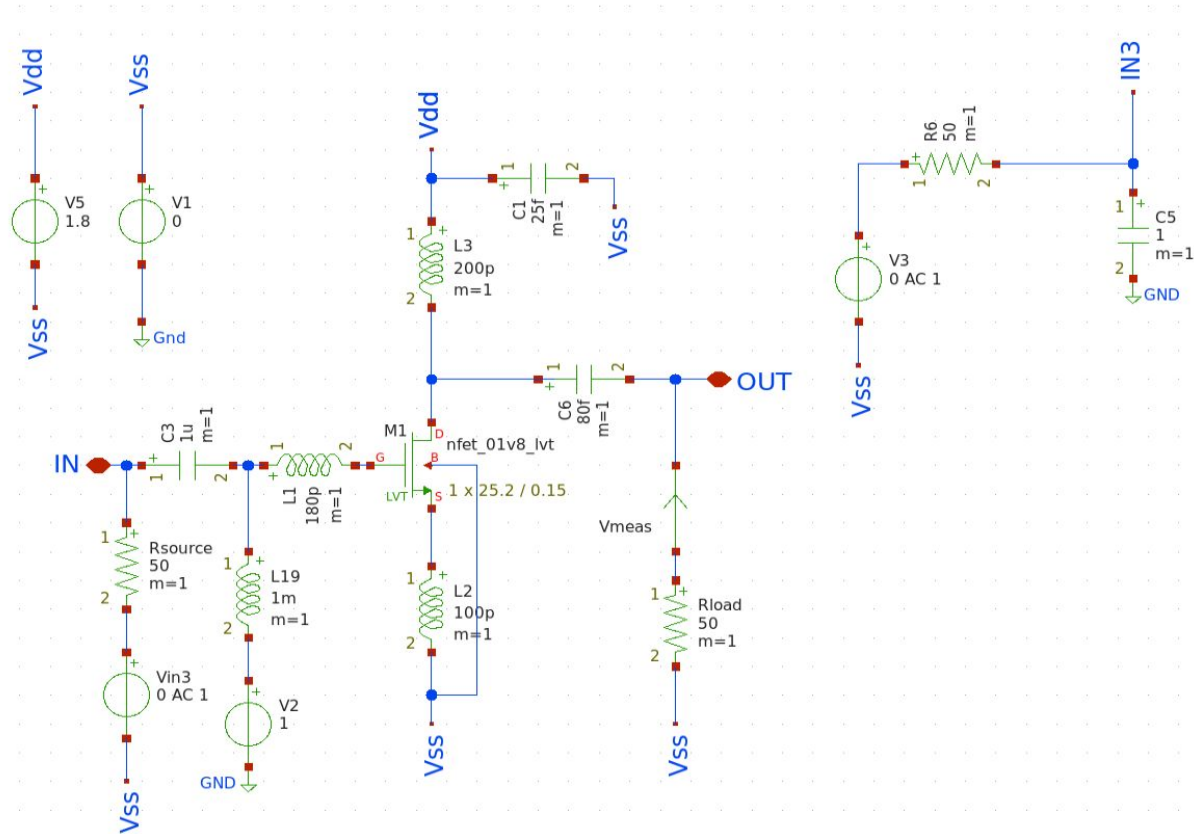- PA first stage test in 1.8V
- $W = 806\mu\text{m}$, $L = 4.8\mu\text{m}$
- Input matched by LG and LS



PA - results


TT_MODELS




s1

```


.save all
.control
op
ac lin 201 50e9 80e9
let S11=2*IN-1
let S21=2*OUT
let S22=2*OUT1-1
let S12=2*IN1
let S33=2*IN3-1
settype s-param S11 S21 S22 S12
let Rbase=50
let delta=(S11*S22)-(S21*S12)
let K=(1-(mag(S11))^2-(mag(S22))^2+(mag(delta))^2)/(2*mag(S12*S21))
let MSG=mag(S21)/mag(S12)*(K-sqrt(K^2-1))
let Y33=(1/50)*(1-S33)/(1+S33)
let freq=im(Y33)/(2*3.1415)
let Y11=((1-S11)*(50+S22*50)+S12*S21*50)/((50+S11*50)*(50+S22*50)-S12*S21*50*50)
let Y22=((1-S22)*(50+S11*50)+S12*S21*50)/((50+S11*50)*(50+S22*50)-S12*S21*50*50)
let Y21=(-2*50*S21)/((50+S11*50)*(50+S22*50)-S12*S21*50*50)
let Y12=(-2*50*S12)/((50+S11*50)*(50+S22*50)-S12*S21*50*50)
let Z11=Y11/((Y11*Y22)-(Y21*Y12))
let Z22=Y22/((Y11*Y22)-(Y21*Y12))
save S11 S12 S21 S22
wrs2p transPA1_2p.s2p
.endc
    
```

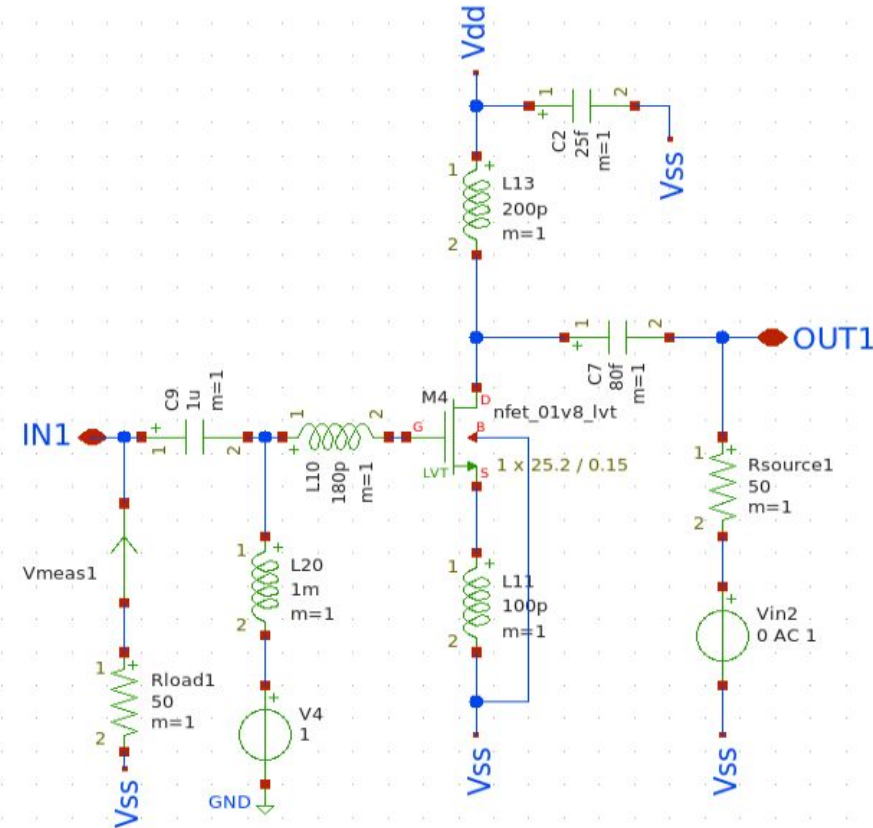

PA - results

 

PA - results

 


PA – next steps

Output matching need to be stage to stage

Plan: create a new testbench to first stage
matched the output

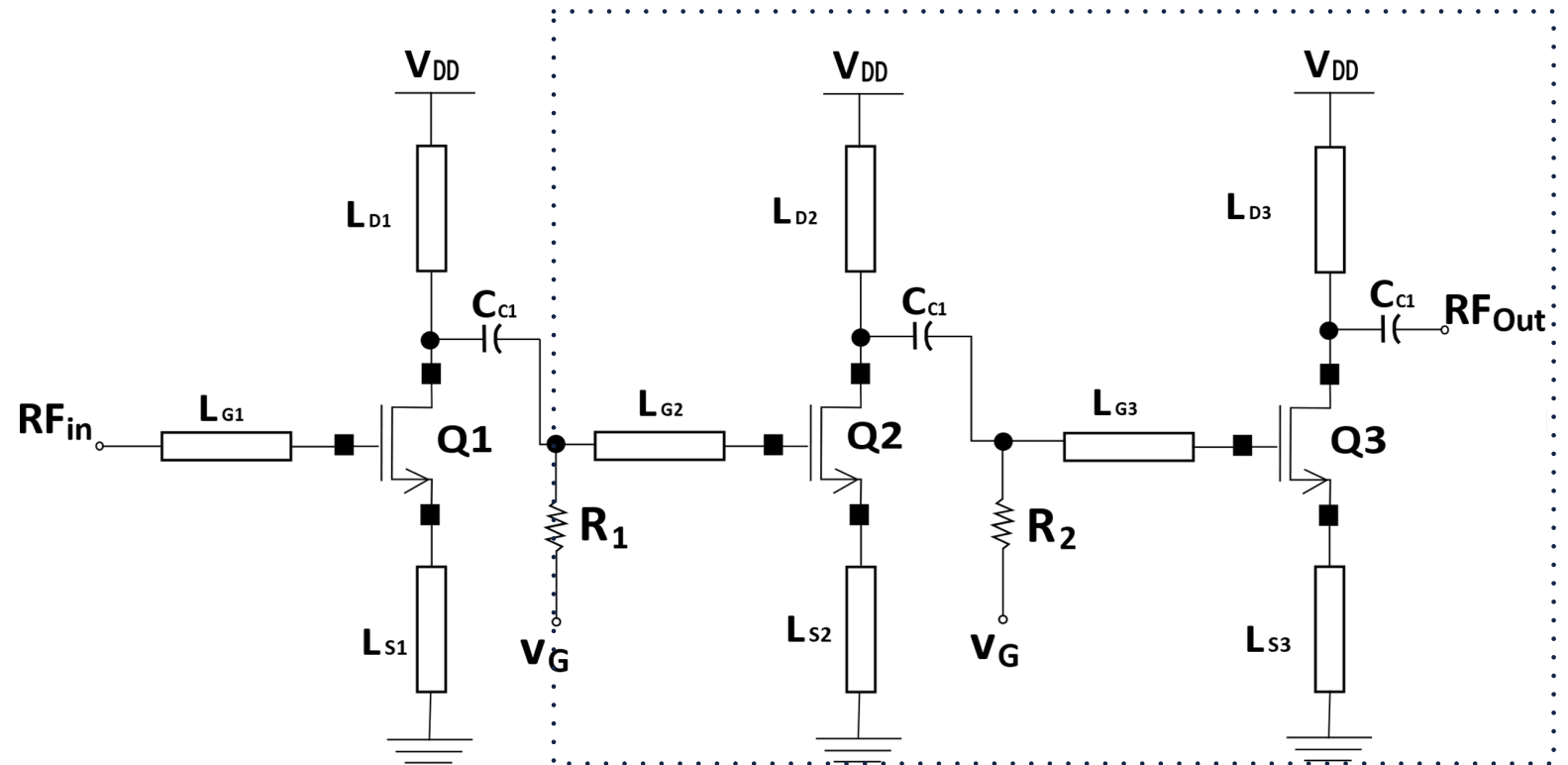for second stage to matched, and after all
schematic design a conjugate matching
network




Low Noise Amplifier - LNA

The presented RF/Analog block - LNA for the specific frequency of 60GHz is a viable option for new uses in bands such as Automotive and telecommunications applications. Although it is a challenging project, especially considering elements not present in commonly used bands, a standardized and widely known procedure is followed, the use of simulation tools and the available PDK opens new ways and forms for tests and prototypes of this type, at its In turn, it shows inconveniences that allow to document and consider for future new versions.

LNA - noise considerations



Transistor sources:

 - Drain noise (thermal and flicker ($1/f$))
- Gate noise (routing parasitic, induced)
- Multiple fingers are recommended



LNA - LCTANK

  - To increase the Q factor: $\uparrow R_{op}$; add series inductor with L_{op}



$$R_{op} = R_{os}(1 + Q^2)$$

$$\omega_o = 2\pi f_o$$


$$R_{os} = \frac{\omega_o L_{os}}{Q_{out}} \quad C_{op} = \frac{1}{\omega_o^2 \cdot L_{op}}$$

$$L_{op} = L_{os}(1 + 1/Q_{out}^2)$$

$$C_{os} = C_{op}(1 + 1/Q_{out}^2)$$





LNA - LCTANK

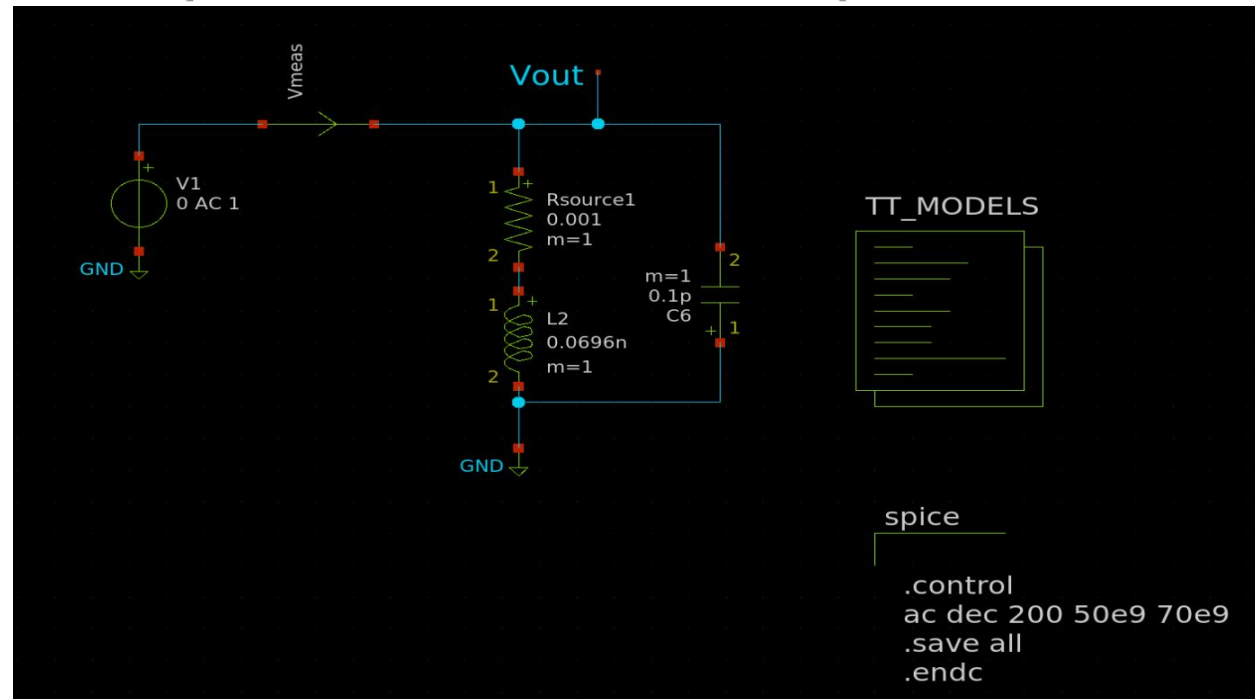- ■ To increase the Q factor: $\uparrow R_{op}$; add series inductor with L_{op}




LNA - LCTANK

   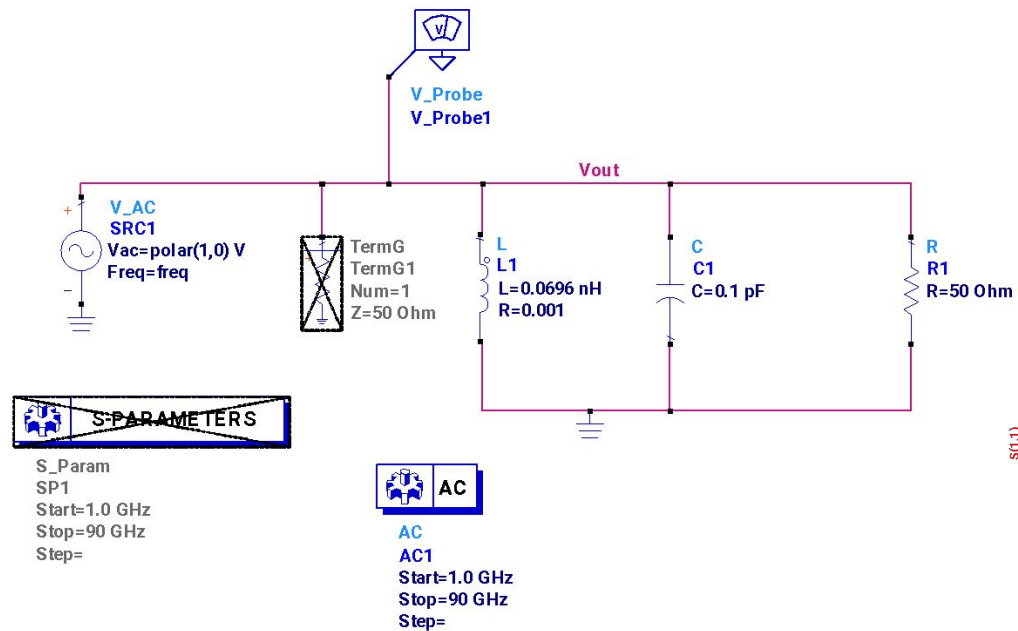- To increase the Q factor: $\uparrow R_{op}$; add series inductor with L_{op}




LNA - INPUT BIASING - T BIAS

- T bias, ratio : 1000 @60GHz

 

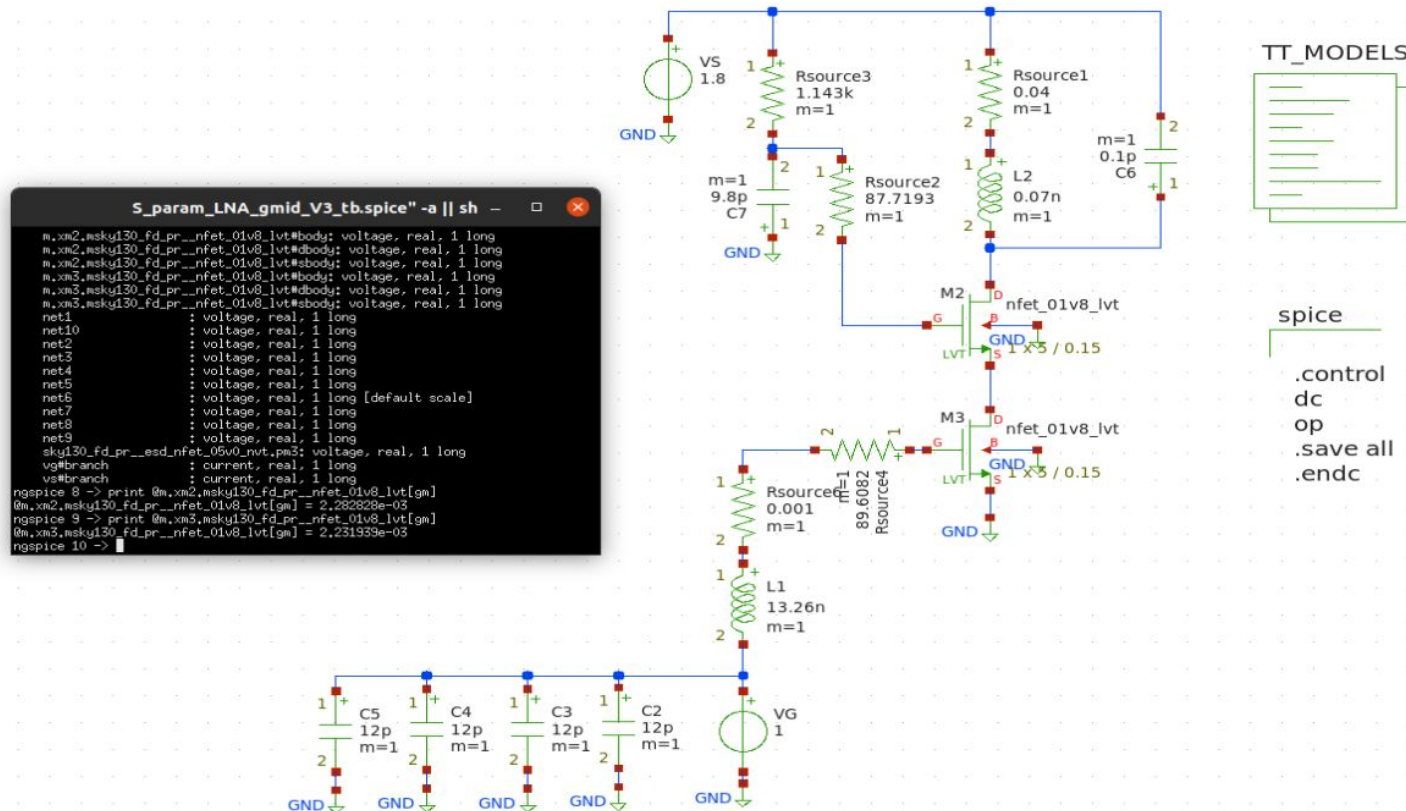LNA - DC OP CONDITIONS: NON QUASI STATIC ANALYSIS




$$R_{source2} = \frac{1}{5 \times gm_{M2}}$$

$$R_{source4} = \frac{1}{5 \times gm_{M3}}$$

LNA - MATCHING

$$G_{max}(\Gamma_S, \Gamma_L, S) = \frac{P_{av,out}}{P_{del,in}} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1}), K \geq 1$$

K=Rollet stability factor

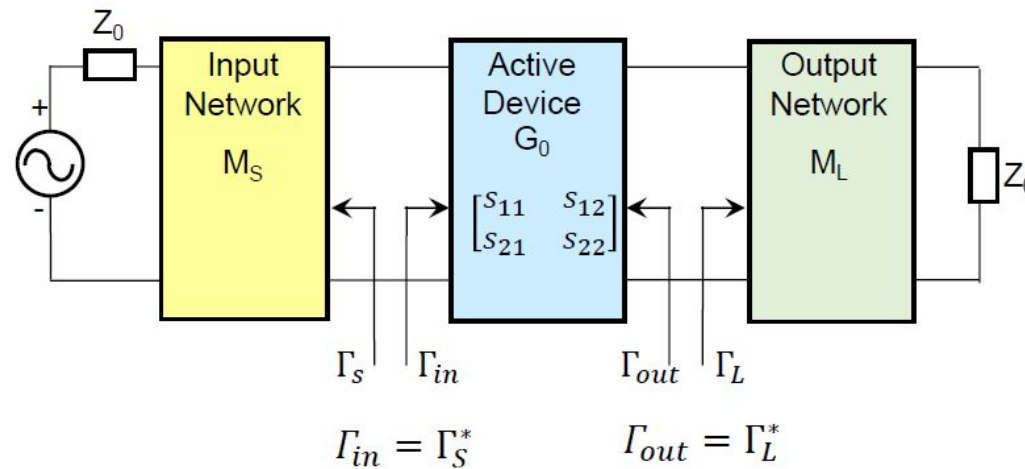

$$Z_{in} = 110.57 - j440.981[\Omega]$$

$$Z_{out} = 13.622 - j25.788[\Omega]$$


Simultaneous conjugate matching



$$\Gamma_S = 0.948 \angle 12.2^\circ$$


$$\Gamma_L = 0.65 \angle 122.6^\circ$$

LNA - MATCHING

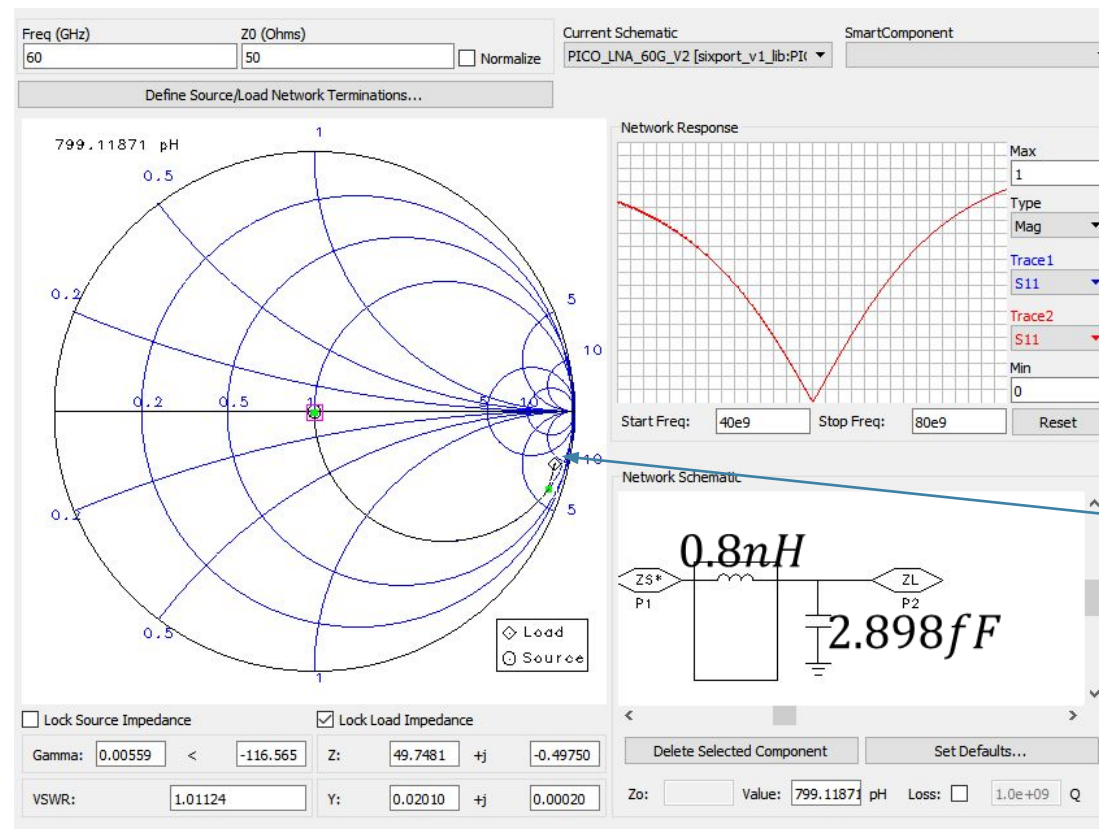


$$Z_{in} = 110.57 - j440.981[\Omega]$$


LNA - MATCHING

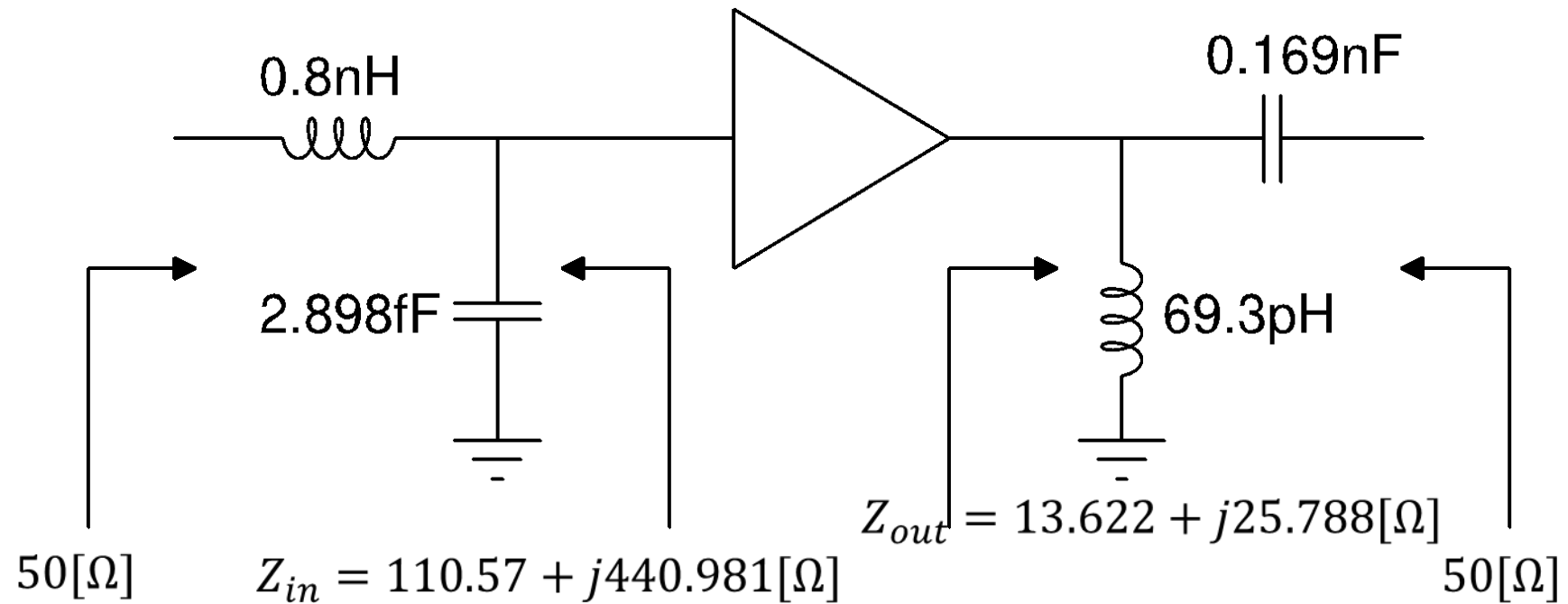

LNA - MATCHING

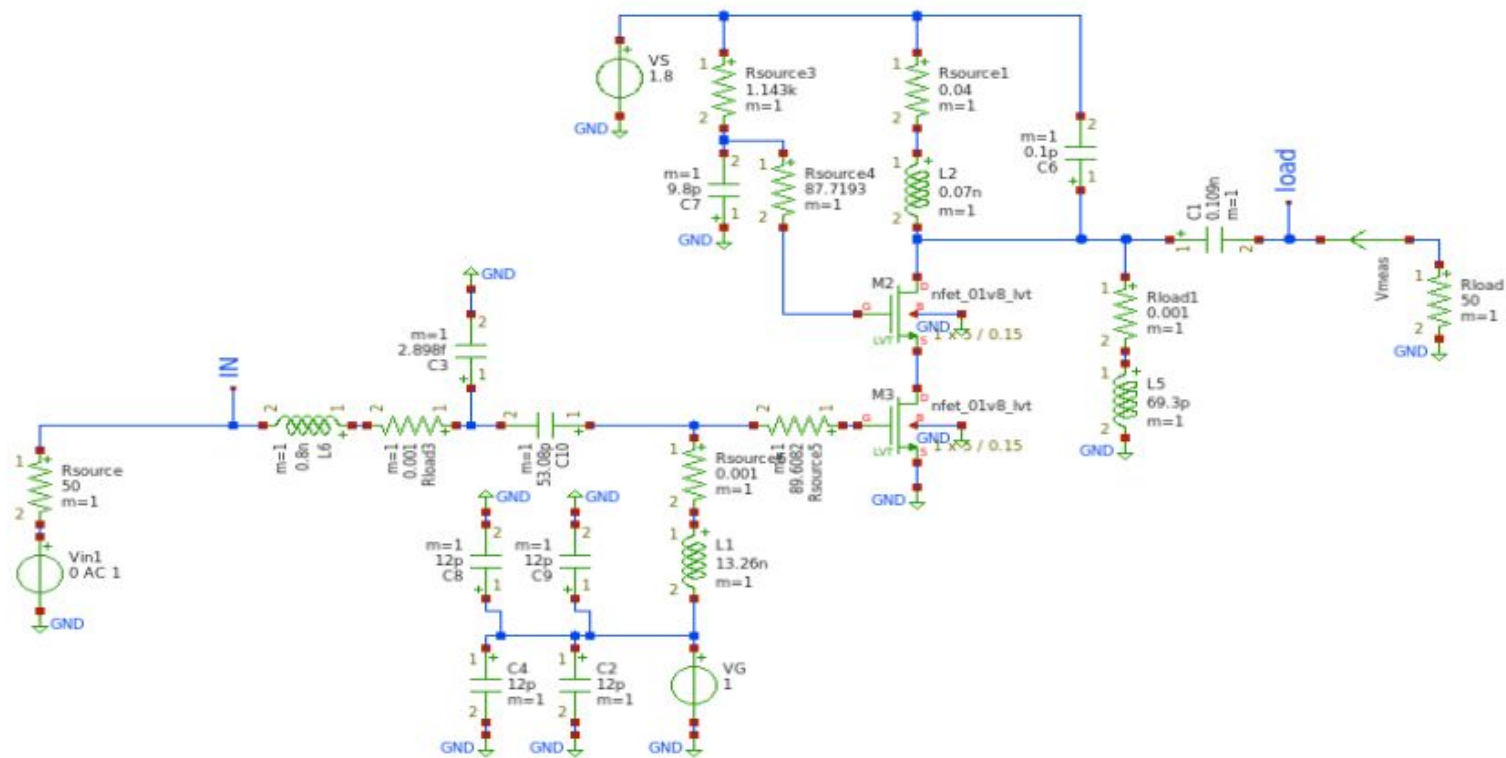

LNA - results

 


S(11) @60GHz	-19.75 dB
S(22) @60GHz	-7.48 dB
S(21) @60GHz	12 dB

LNA - next steps

- Procedure for noise analysis in Xschem.
- Add gm/Id analysis for amplifier gain improvement.
- Replace ideal models by micro stripline sub-blocks.
- Post layout simulations.
- Inter-blocks integration in layout.
- Post layout stability circles analysis.

LNA - early layout

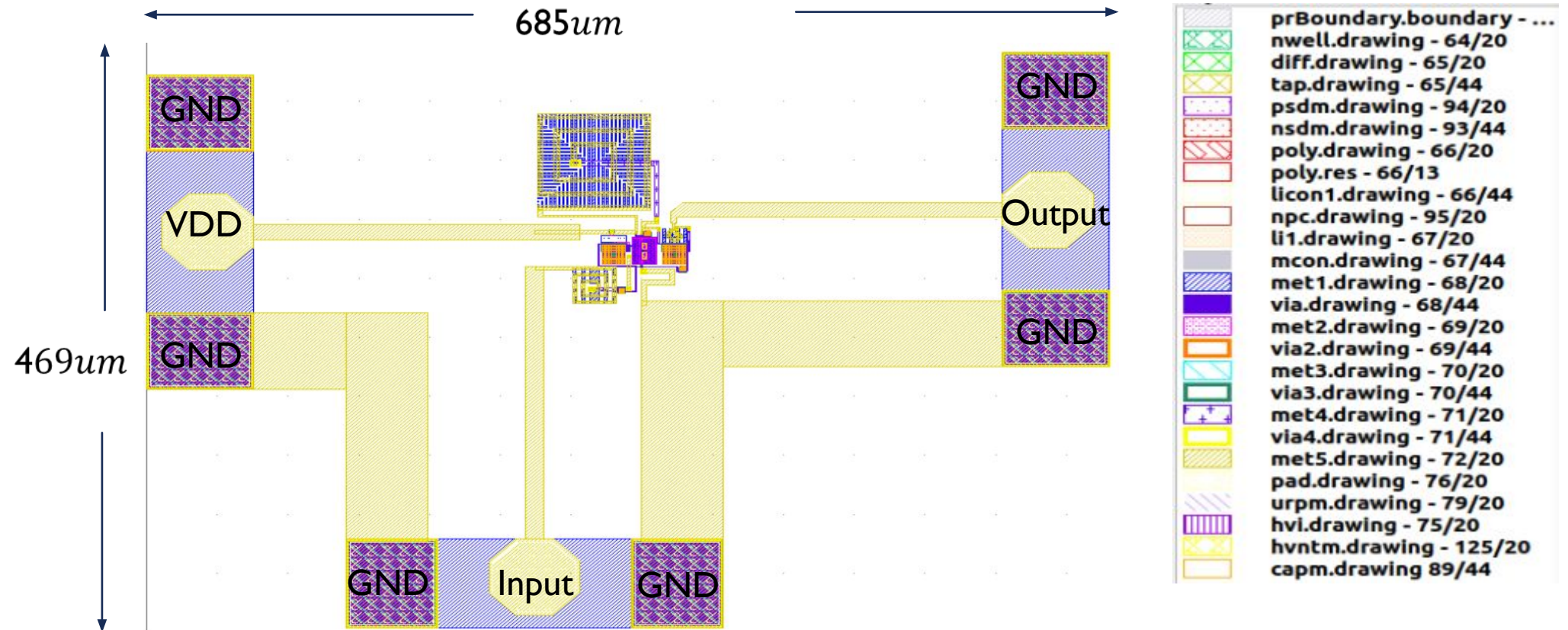

References

- [S1] S.-F. Chao, H. Wang, C.-Y. Su and J. G. J. Chern, "A 50 to 94-GHz CMOS SPDT switch using traveling-wave concept", IEEE Microw. Wireless Compon. Lett., vol. 17, no. 2, pp. 130-132, Feb. 2007.
- [S2] R. Shu and Q. J. Gu, "A transformer-based V-band SPDT switch", IEEE Microw. Wireless Compon. Lett., vol. 27, no. 3, pp. 278-280, Mar. 2017.
- [S3] R.-B. Lai, J.-J. Kuo and H. Wang, "A 60–110 GHz transmission-line integrated SPDT switch in 90 nm CMOS technology", IEEE Microw. Wireless Compon. Lett., vol. 20, no. 2, pp. 85-87, Feb. 2010.
- [S4] A. Tomkins, P. Garcia and S. P. Voinigesu, "A passive W-band imaging receiver in 65-nm bulk CMOS", IEEE J. Solid-State Circuits, vol. 45, no. 10, pp. 1981-1991, Oct. 2010.
- [S5] L. Chen et al., "A 90-GHz asymmetrical single-pole double-throw switch with >19.5-dBm 1-dB compression point in transmission mode using 55-nm bulk CMOS technology", IEEE Trans. Circuits Syst. I Reg. Papers, vol. 68, no. 11, pp. 4616-4626, Nov. 2021.
- [S6] L. Chen, L. Chen, Z. Ge, Y. Sun, T. Hamilton and X. Zhu, "A W-Band SPDT Switch With 15-dBm P1dB in 55-nm Bulk CMOS," in IEEE Microwave and Wireless Components Letters, vol. 32, no. 7, pp. 879-882, July 2022, doi: 10.1109/LMWC.2022.3159529.
- [S7] J. He, Y. -Z. Xiong and Y. P. Zhang, "Analysis and Design of 60-GHz SPDT Switch in 130-nm CMOS," in IEEE Transactions on Microwave Theory and Techniques, vol. 60, no. 10, pp. 3113-3119, Oct. 2012, doi: 10.1109/TMTT.2012.2211380.

OUR DESIGNS AND CARAVEL

- Estimated total area of all our circuits (plus test devices): 4 mm²
 - The 5 circuits presented here will be laid out to make most use of the area and to accommodate the contributions of teams USAI and Austria
 - The test devices, which are very compact, will be placed in the empty spaces
- Number of pins after sharing:
 - 5 caravel analog pins
 - 3 GPIOs used as analog
- For the “internal” pin share, there are two options:
 - 1) Group the 5 circuits in two larger blocks (LNA+PA+VGA and Switch+VCO) to only use the 8 pins available
 - 2) Lay out each circuit and add an extra ground pad inside the layout of each circuit
- Pin routing will be done as follows:
 - For low impedance inputs and outputs: routing will be done in M5 to minimize IR drop
 - For high impedance inputs: routing will be done in M3, using M4 as interconnection layer

OUR DESIGNS AND CARAVEL

- Layout strategy for devices
 - MOSFET: multi-finger layout to improve performance in mmW
 - MIM capacitor: accesses done in the topmost metal of the device (M4 or M5), ground plane cut beneath the capacitor to reduce parasitic shunt capacitance to ground or substrate. A guard ring will be studied.
 - MOM capacitors, if needed, will be laid out in a completely custom way, also with guard ring and shield
 - SCPW, planar inductors: custom layout based on their design and simulation results, avoiding routing signals in LI because of its high sheet resistance. Inductors will receive custom LI+P+ guard rings to reduce substrate currents
 - MOS varactor: varactor bank will be laid out using multiple devices in parallel, gate as fixed bias, source/drain as bias input, substrate guard ring on each varactor to minimize cross-talk
 - Poly resistors: input and output in M1, guard ring grounded to reduce substrate currents

PLAN FOR NEXT WEEKS

- Chipathon deadlines
 - October 31st - circuits (almost) ready for tape-out
 - November 14th - tape-out deadline
- Our deadlines
 - October 7th - Active cells and passives laid out, DRC + LVS clean and PEX
 - October 14th - Final design ready, DRC + LVS clean locally
 - October 21st - Top cell DRC+LVS clean, mock caravel placement ready
 - October 28th - Buffer week to solve bugs and other (or any) unforeseen problems
 - November 4th - Coordinate with USAI and Austria the final circuit placement plus pin routing
 - November 11th - Placement+routing ready, final pre-check ready
 - November 14th - The big day

LAYOUT STRATEGIES

- Active blocks: M5 inputs and outputs, M1 ground plane, Minimize ground inductance and propagation losses. MOSFETs have $f_t \sim 70$ GHz, which pose real design issues. Thus, minimizing parasitics is paramount. This means that we're willing to sacrifice matching to reduce parasitics.
- Passive blocks: M5 signal, M1 ground (for microstrip-like structures and inductors), M1 or M2 for floating shield (SCPW). Since the metals are thin (1.2 μm for M5, 845 nm for M4-3, 360 nm for M2-1) and not copper (which has about half of aluminum's resistivity), reducing propagation losses in the form of ohmic losses is paramount. Thus, M5 will be used as signal, and whenever possible, a M5+M4 combination will be studied.